

The schematic shows a 220VAC input connected to a motor (M) and a speed control circuit. The speed control circuit includes a TRIAC (T1, 400V-10A), a DIAC (D1), a potentiometer (P1), and several resistors (R1, R2, R3, R4, R99, R100). The motor is connected to the output of the TRIAC.


## AC Motor Speed Controller Circuit

RECEIVED BY EMAIL

motor controllers   triac

This triac-based 220V AC motor speed controller circuit is designed for controlling the speed of small household motors like drill machines. The speed of the motor can be controlled by changing the setting of P1. The setting of P1 determines the phase of the trigger pulse that fires the triac. The circuit incorporates a self-stabilizing technique that maintains the speed of the motor even when it is loaded.
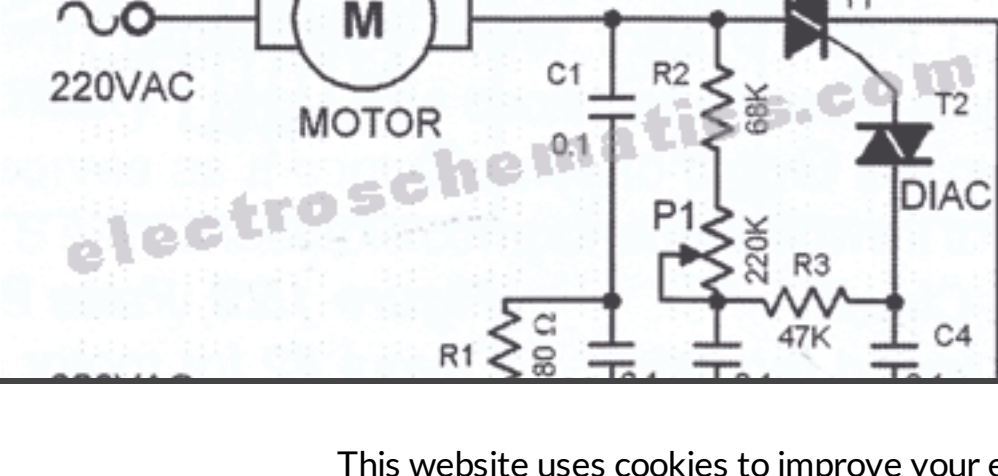
### 220VAC Motor Speed Controller Schematic



This website uses cookies to improve your experience. We'll assume you're ok with this, but you can opt-out if you wish.


Accept

Read More


For example, when the motor of the drill machine is slowed down by the resistance of the drilled object, the counter-EMF of the motor also decreases. This results to a voltage increase in R2-P1 and C3 causing the triac to be triggered earlier and the speed increases accordingly.

Related Products: [Motors](#) | [AC Motors](#) | [Brushless DC Motors](#)
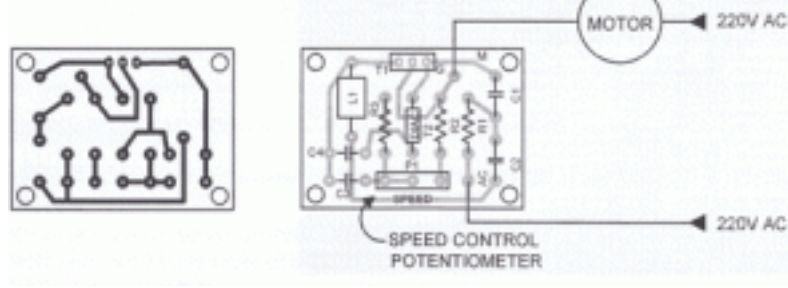
### Printed circuit board layout of the motor speed controller



Another version found [here](#).

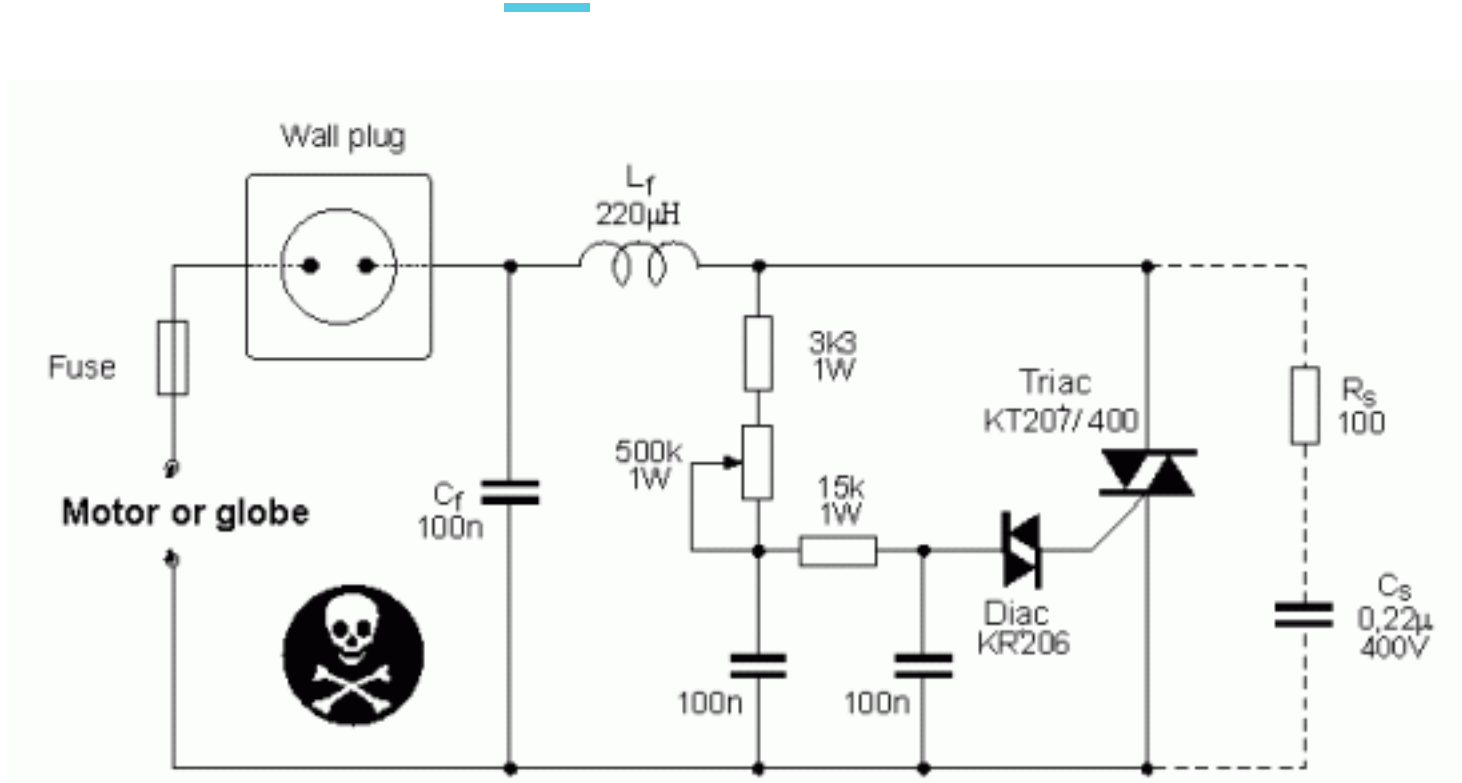

If the main use for this circuit is to control the brightness of a light bulb, RS and CS are not necessary.

Previous

LM567 Infrared Transmitter Circuit

Next

MC1458 Datasheet

### Related Tutorials

No related posts.

Multiple RTL 2832U dongles in one radio
ripple voltage
i need to interface r c circuit with the internal ADC pin of pic controller
systematic diagram is needed
systematic diagram is needed


### Recent Posts

- [Arduino Powered PIR Motion Detection Light](#)
- [An Ultrasonic Shortcut – Getting the HC-SR04 Transducer Up and Running Fast!](#)
- [Poor Man's Peltier Mini Fridge – Part 1 of 2](#)
- [MP2307 Digital Power Supply Module: Teardown Analysis Part 2/2](#)
- [The Tiny Tesla Coil – DIY](#)

## 89 Comments
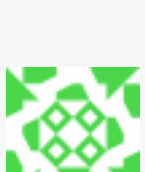
### Join the conversation!

You must be [logged in](#) to post a comment.



vougiouklis

I would like to congratulate and thank you for your WWW.

Please forgive my naivety for my questions.

- I hope to use the SC to slow down a fan 45 Watts, may I use the ordinary small parts used by amateurs?
- I found a discrepancy between the diagrams of the main 2 similar images and the small one #4 image.

In the main image L1 on the left is connected with C2 and R1 in the small image is connected with C3 and C4, am I right? what I have to do?

- In the small image R3 ends unconnected.
- I suppose that I have to connect the line to R3, am I right?

Posted on December 17th 2017 | 3:22 pm

Log in to Reply



agustindazagmail-com

Has anyone else noted the noise generated by the AC motor when controlling using a Triac with phase shift?

Has anyone experimented with the Snubber circuit (C1, C2 and R1 in the original circuit above) to try to minimize the electrical noise on the motor?

Any success?

Posted on March 14th 2017 | 7:24 pm

Log in to Reply



shinekprabymail-com

Dear Sir,

Happy new year


I used this circuit in my washing machine, it gets desirable speed for spin but for wash (when I reduced and set the speed in potentiometer) it is not starting as it does not get the required surge. When I move the potentiometer, it runs in more speed then I reduced the speed by turning the potentiometer and switched off the motor. Now the position of the potentiometer is perfect as per the speed I required but when I start it again it does not start as it does not gets enough surge. I have used 500K potentiometer. Can you please suggest, which components should I used to get enough surge in more resistance.

Thanks,

Shine

Posted on December 30th 2016 | 9:01 am

Log in to Reply

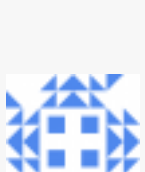


haythem

Hi My Dear I need to control this with Arduino with time can you help me ?

Posted on December 27th 2016 | 9:27 pm

Log in to Reply

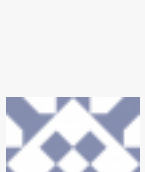

jon-matiszyahoo-ca

just wondering what the values would be for 120v mains and 1hp motor?

I'm going to try to convert a washing machine universal motor to a wood lath drive.

thanks

Posted on July 28th 2016 | 4:09 am

Log in to Reply




ArBiNd

if my P1 is set to a fixed resistance R, will the motor speed be the same for different ac input e.g 220V & 190V?

Posted on January 16th 2016 | 9:59 am

Log in to Reply

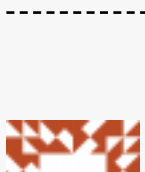

Nikhil

which triac and diac should I use for 2000W heater load, and also value of capacitor. provide ckt if possible

Posted on January 15th 2016 | 11:36 am

Log in to Reply




suleiman

Why the diac , what is the function,

Posted on December 22nd 2015 | 5:57 am

Log in to Reply

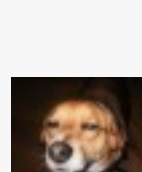

Jim Keith

The DIAC is a triggering device – it blocks until the voltage across it exceeds about 28V – at this point, it breaks over and dumps the charge stored in C4 into the TRIAC gate.

This provides a high current, fast rise time gate pulse.

Posted on December 22nd 2015 | 6:05 am

Log in to Reply




pasan

hi sir .....! this circuit can be drive 1hp or 2hp motors ...?

Posted on December 01st 2015 | 7:15 pm

Log in to Reply

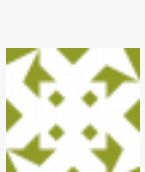

Hossam Zayed

I'm building a project that requires a device to control a 3 phase induction AC motor 1.5 kw and 1400 rpm to do the following

1-reverse Motor direction

2-switch motor on/off (frequency up to 1 time per second)

3- Can be controlled by a micro controller (i.e accepts digital signal)


No need for controlling motor speed

does your circuit design provide the control device I'm looking for?

thanks and waiting for your kind reply

Posted on September 12th 2015 | 7:48 am

Log in to Reply

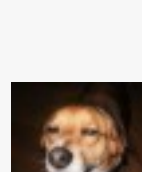

Jim Keith

This circuit is for single phase applications only. I will soon post a circuit that will control a 3phase motor.

Posted on September 14th 2015 | 2:27 pm

Log in to Reply

View More

### Login

Email

### Password

☐ Remember Me

Log In

[Register](#) | [Lost your password?](#)

### Latest Article Comments

#### MP2307 Digital Power Supply Module:

##### Teardown Analysis Part...

"Thank you for inspiring me. I am guessing that you need the design of an adjustable dc dummy"

#### MP2307 Digital Power Supply Module:

Is"

#### Working with Water Flow Sensors &...

"We are also flow sensor manufacturer in Pune. We are AQUA KREELA which is in manufacturing of 3/4"

#### Poor Man's Peltier Mini Fridge – Part 1 of...

"Adam Carlson: I'm sure you can develop nifty ideas using these wonder chips. Please take a look at"

#### Poor Man's Peltier Mini Fridge – Part 1 of...

"I have always been fascinated by these devices. I have never really gotten out to play with one"

View More

### New Projects

### Recent Q&A

Arduino Powered PIR Motion Detection Light

An Ultrasonic Shortcut – Getting the HC-SR04 Transducer Up and Running Fast!

Poor Man's Peltier Mini Fridge – Part 1 of 2

MP2307 Digital Power Supply Module: Teardown Analysis Part 2/2

The Tiny Tesla Coil – DIY

## Stay Up To Date

SUBSCRIBE

### Popular Tags

- IC datasheet
- LED
- audio amplifier
- battery chargers
- 741
- fm transmitters
- solar chargers
- AVR tutorial
- led flashers
- arduino tutorial

