

# 11061 PGN

## Power, Ground and Noise

# Class Objective

## When you finish this class you will:

- Understand the importance of considering noise early in the design cycle
- Understand the nature of electrical noise
- Observe the impact of good design practice
- Know where to find additional resources from the website and EMC community at large


# Agenda

- **Consequences of Designing with no Regard to Noise**
- **Areas to Concentrate on**
  - Device Noise
  - Conducted Noise
  - Radiated Noise
- **Test Results of a Good Design**



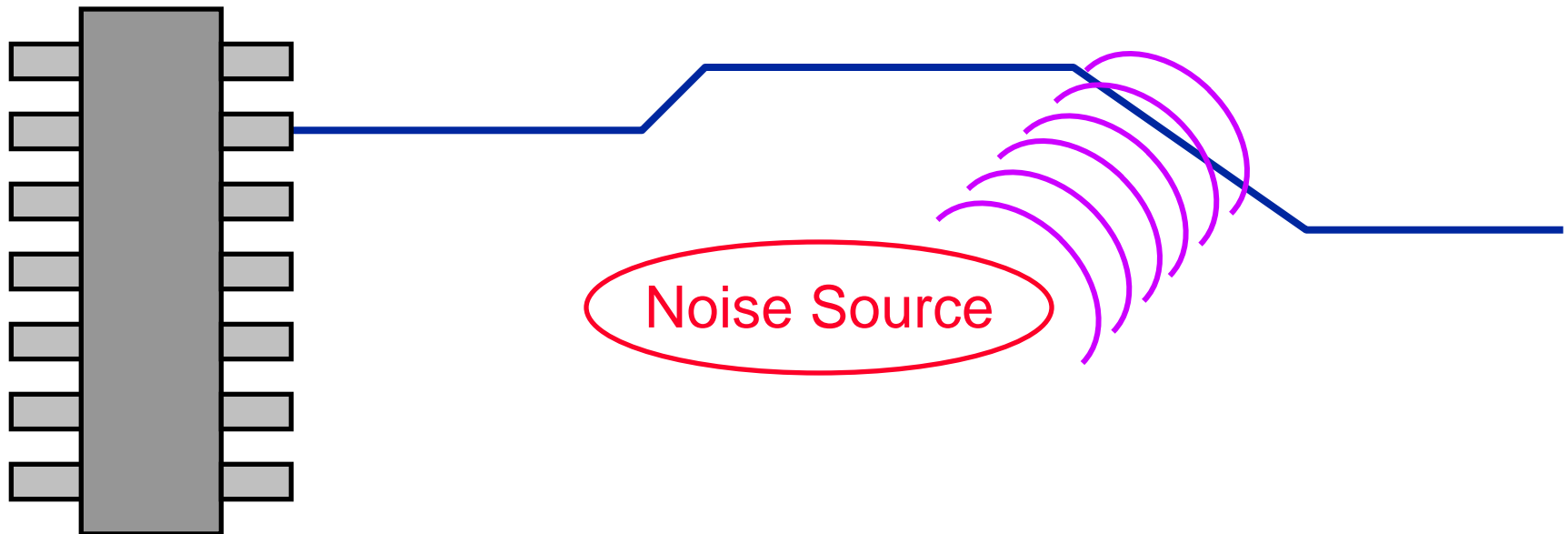
# Long Traces: Antenna

- A trace going into an ADC input longer than a few inches is a potential antenna



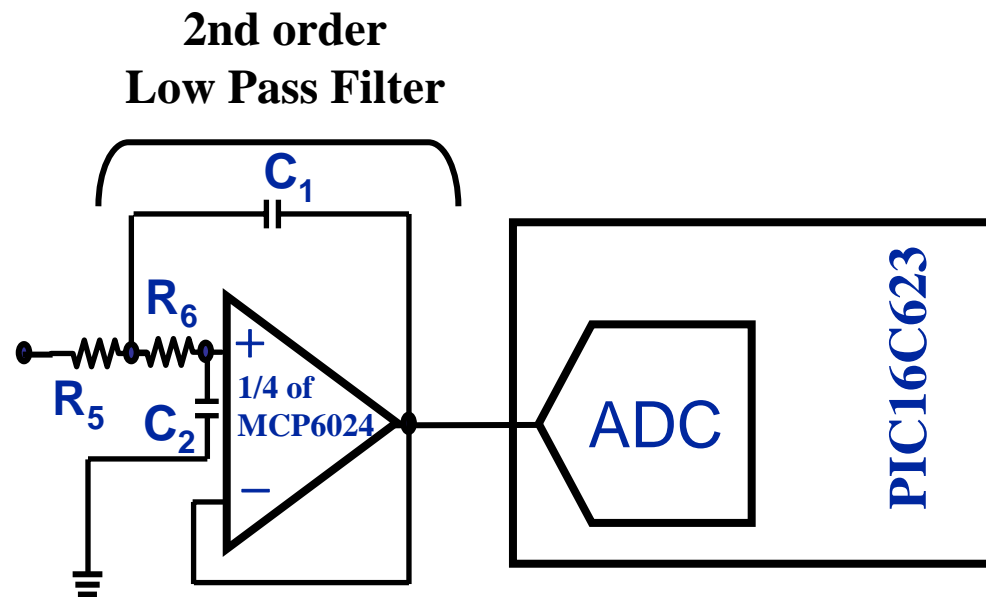
# Low-Pass Filter Missing

- Traces going into ADC inputs longer than a few inches
- No anti-aliasing (or Low-Pass) Filter at the input of the ADC



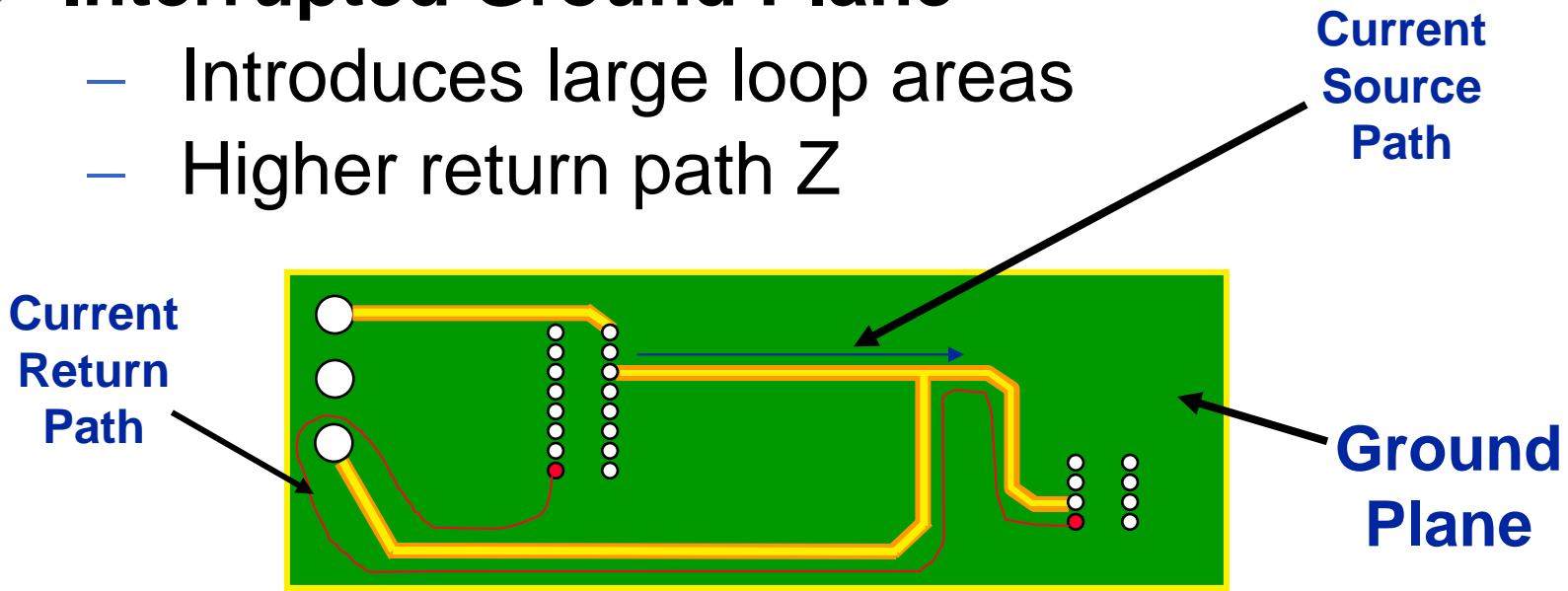
# Discontinuous Ground Plane

- Traces going into ADC inputs longer than a few inches
- No anti-aliasing (or Low-Pass) Filter at the input of the ADC
- Interrupted Ground Plane
  - Introduces large loop areas
  - Higher return path  $Z$




# Application Board #1 (top side)

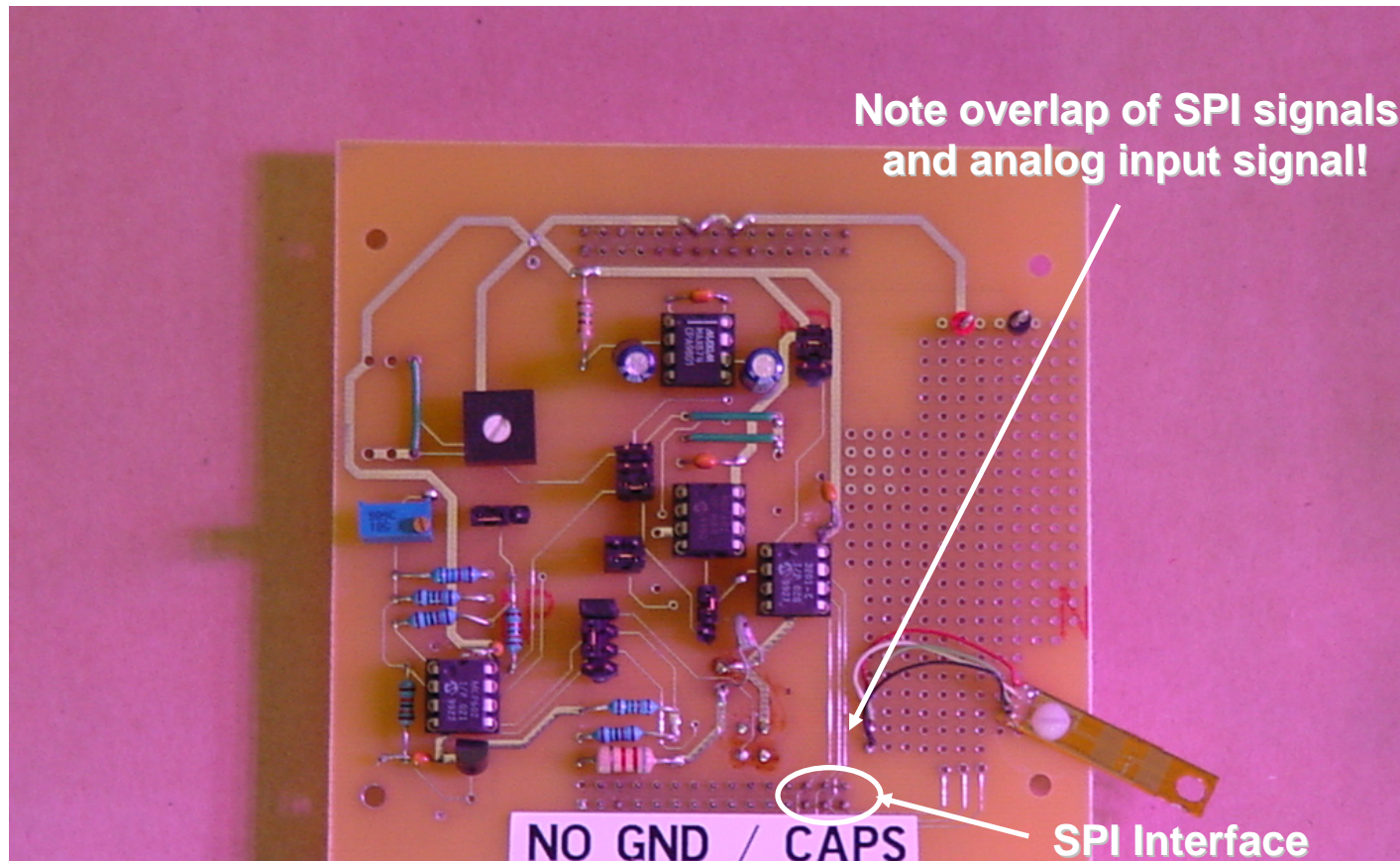

HIGHER VALUE RESISTORS / NOISY AMPLIFIER /  
NO BY-PASS CAPS / NO LP FILTER / NO SUPPLY CHOKE




# Application Board #1 (bottom side)

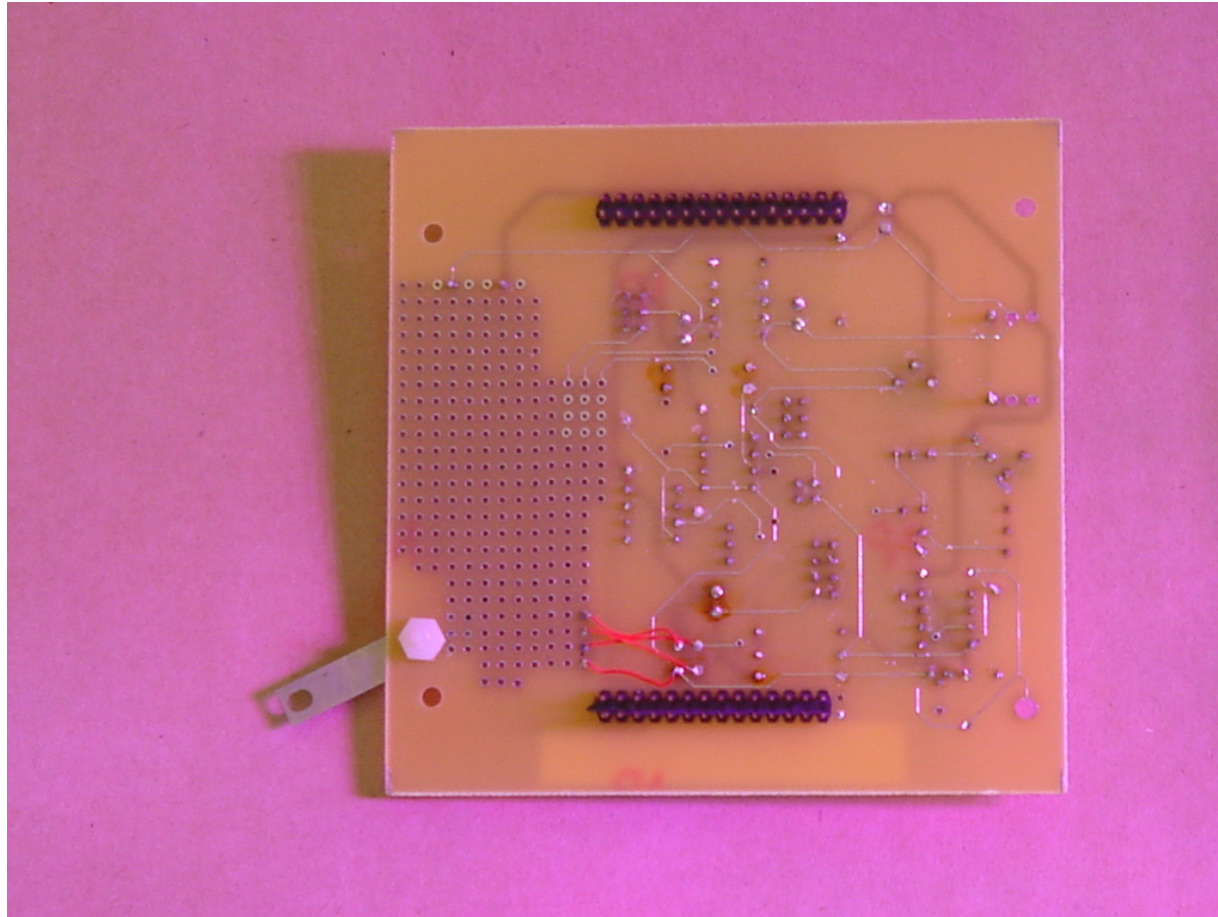

**NO GROUND PLANE**

# Application Board #1 Test Results

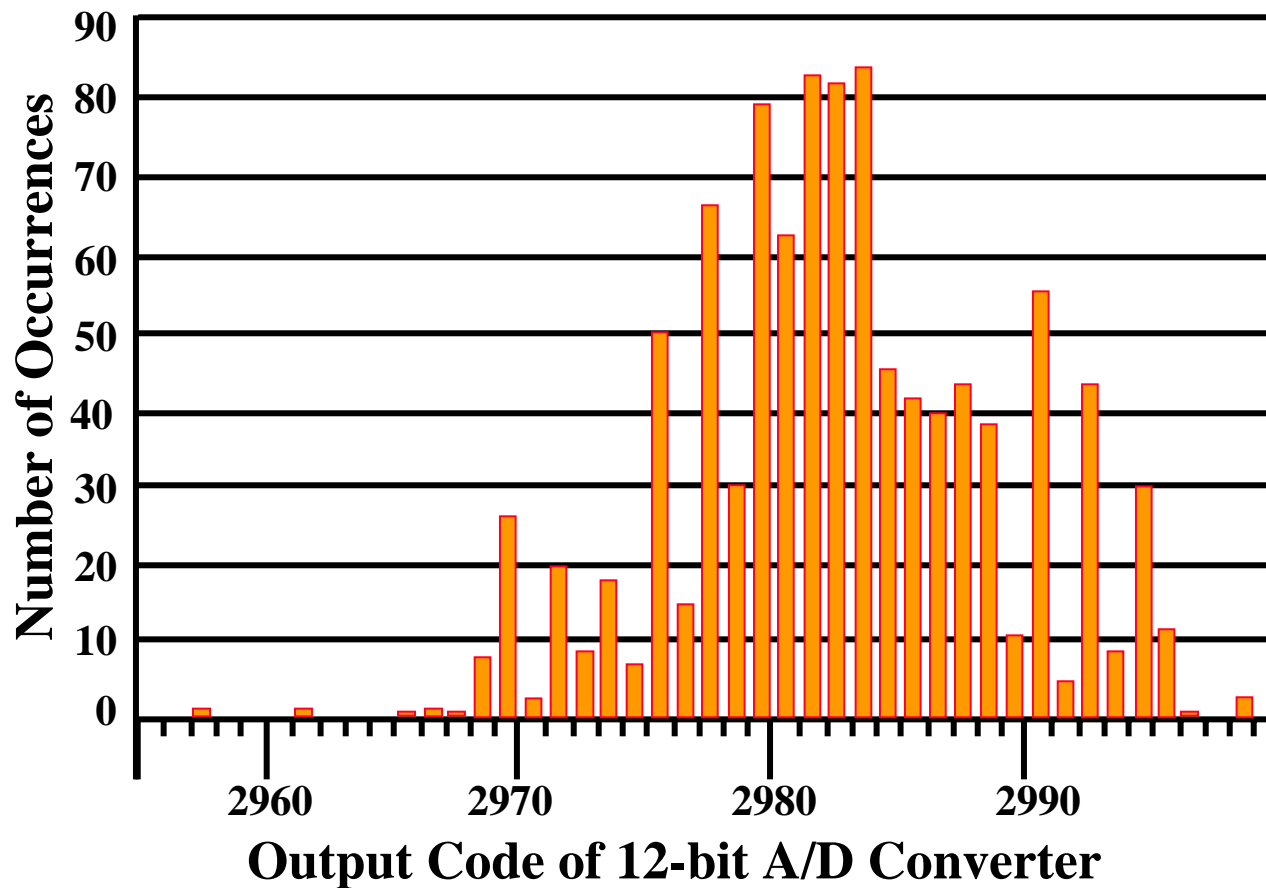

**Code Width  
of Noise = 44**

**(total samples = 1024)**

# Low Noise Design

- **Device Noise – Created by the devices**
  - Resistors - Reduce Values where possible
  - Op amps - Use Lower Noise Amplifiers
- **Radiated Noise – Externally Generated**
  - Reduce trace loop areas within sensitive circuitry
  - Environment - Shield or change orientation
  - Filter low-level Signal traces
- **Conducted Noise – In the Circuit Traces**
  - Use a Continuous Ground Plane
    - Apply 'moat' concept to isolate digital & analog planes as needed
  - Layout - Keep analog and digital Separate
  - Filter low-level Signal traces
  - Filter/Decouple Supply traces
  - Power Supply - Replace Switching Devices


# Device Noise

## ● Resistors

- Johnson or Thermal Noise
- $V_{RN} = \sqrt{4KTR(BW)}$  {Vrms}
- K = Boltzman's Constant =  $1.38e^{-23} \text{ JK}^{-1}$
- T = Temperature in Kelvin
- R = Resistance in Ohms
- (BW) = Noise Bandwidth in Hz
- $1\text{k}\Omega = 4\text{nV} / \sqrt{\text{Hz}}$

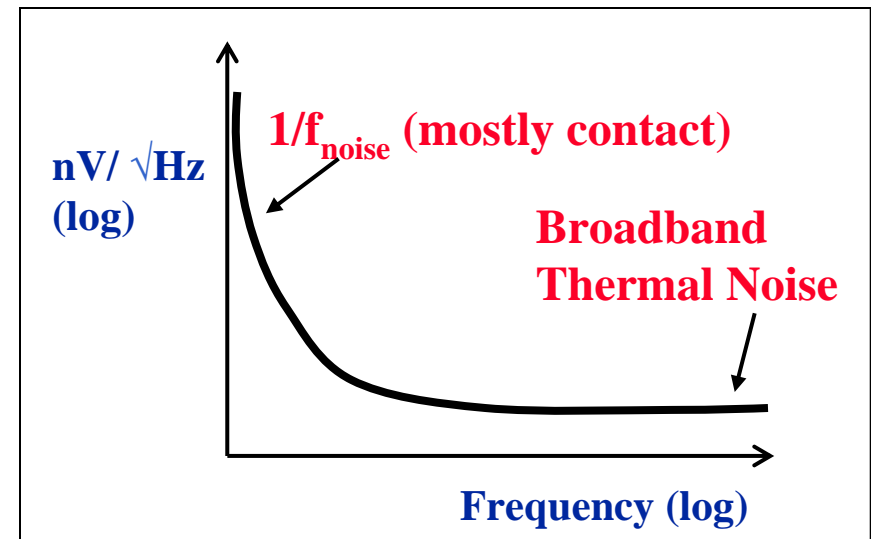
## ● Amplifiers

- MCP602 Specification -  
 $29\text{nV} / \sqrt{\text{Hz}} @ 1\text{kHz}$
- MCP6022 Specification -  
 $10\text{nV} / \sqrt{\text{Hz}} @ 10\text{kHz}$


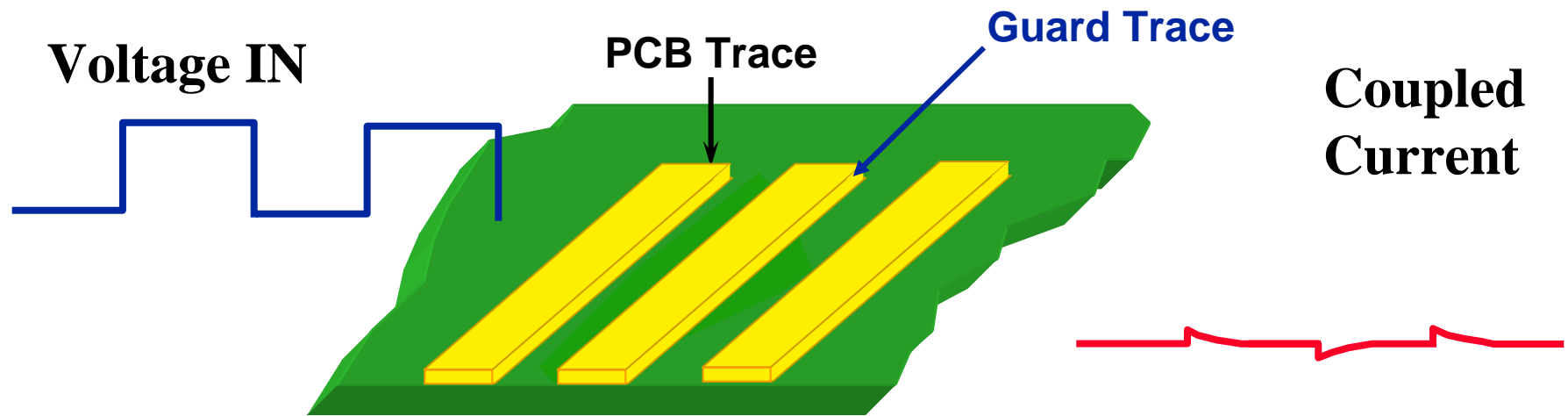
# Coupled Noise (Crosstalk)

- Decrease “L” or Increase “d”
- Put Ground Guard Between Traces



$$C = \frac{w \cdot L \cdot \epsilon_0 \cdot \epsilon_r}{d} \quad \text{pF}$$

$$I = C \frac{dV}{dt} \quad (\text{amps})$$


# Application Circuit

## 12-bit Accurate Circuit Components

$R_3 = 30k\Omega$ ,  $R_4 = 10k\Omega$ ,  $R_G = 402\Omega$ , (+/-1%)


MCP6022 = Single Supply, CMOS, low noise, dual op amp

MCP3201 = 12-bit, A/D SAR Converter

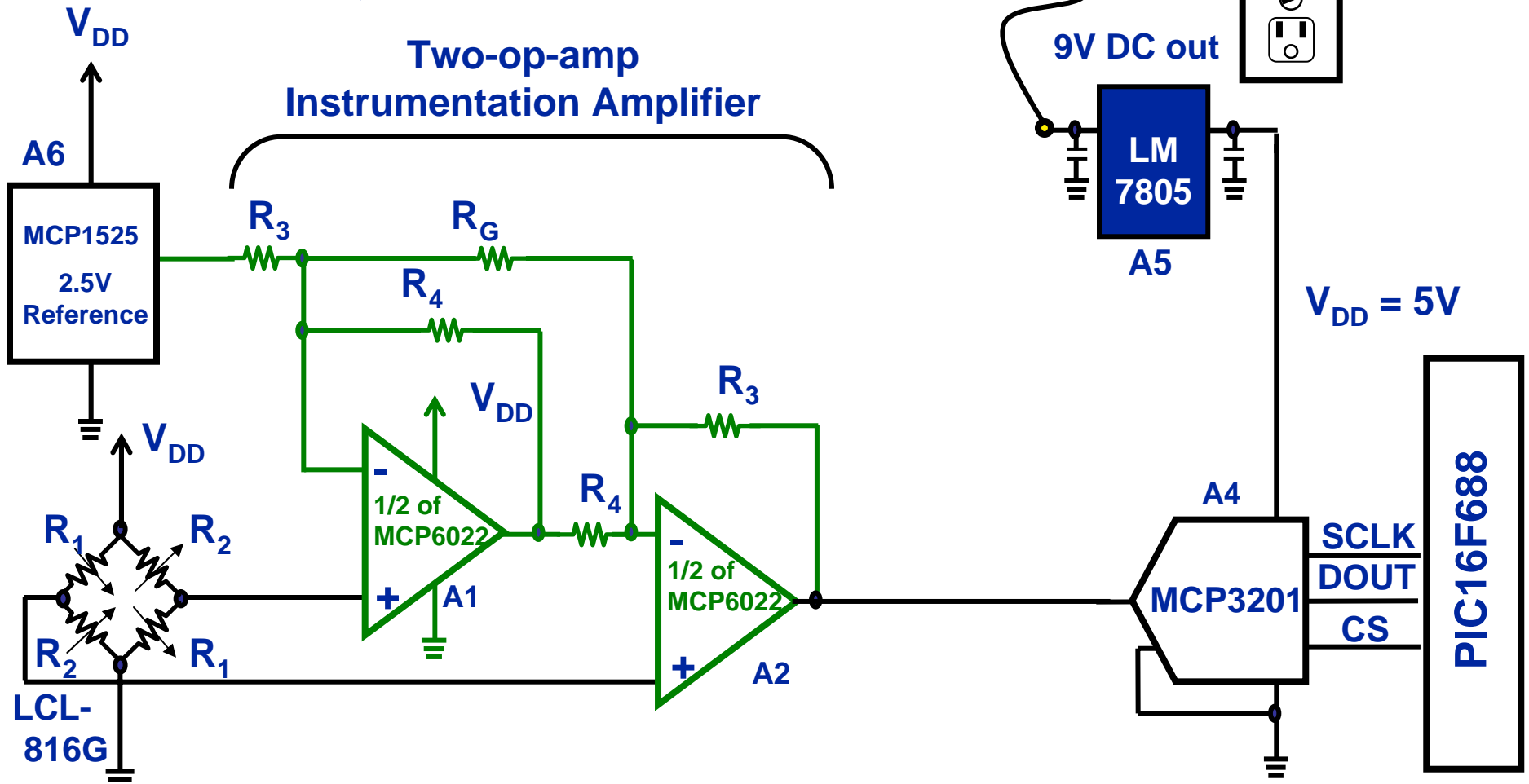



# Application Board #2 (top side)

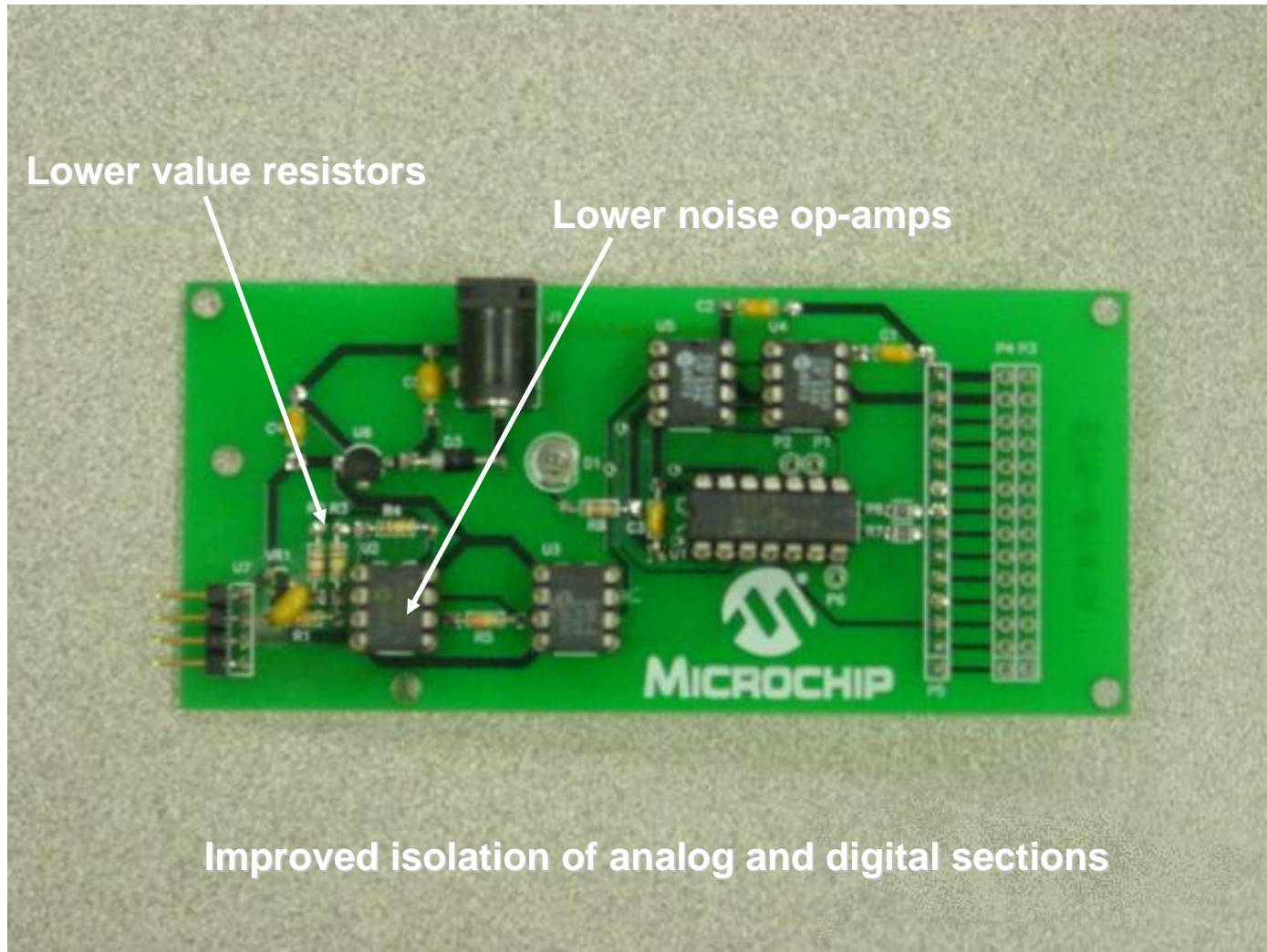

# Application Board #2 (bottom side)






# App Board #2 Test Results

Code Width of Noise = 6

(total samples = 1024)

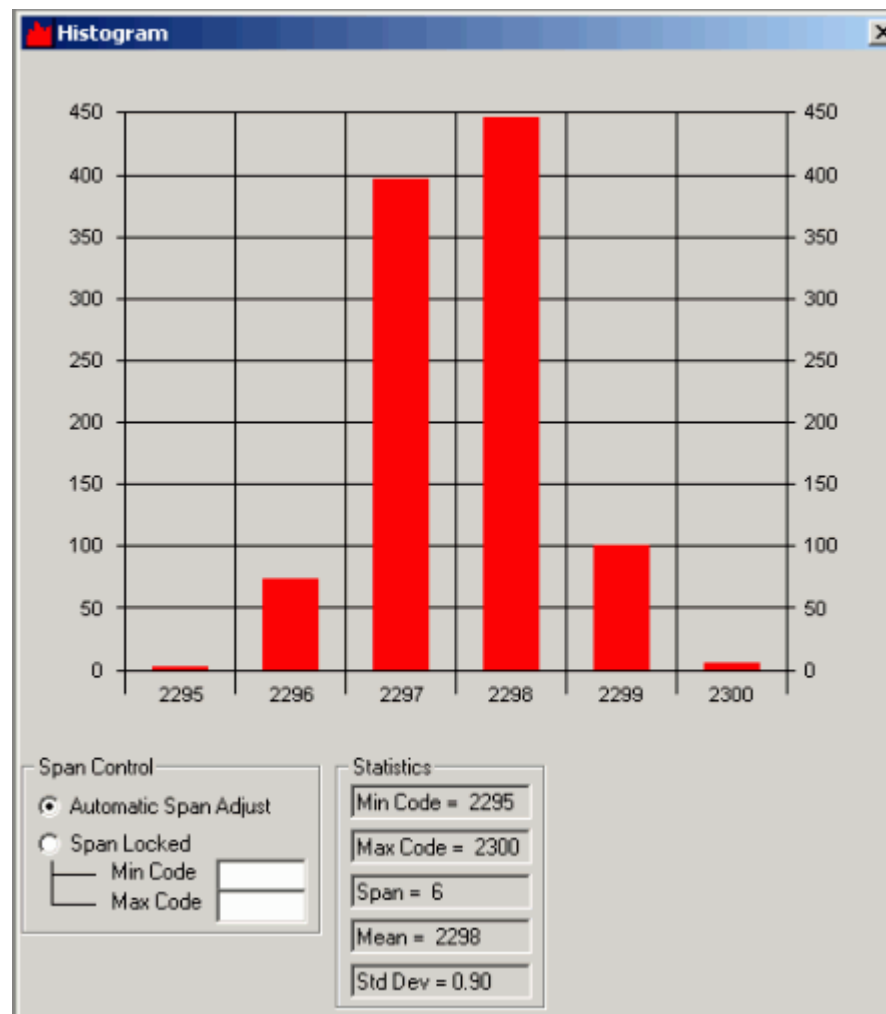- Causes:
  - Environmental 50/60Hz noise on inputs
  - PCB common mode noise



# Conducted Noise

- **Ground and Power**

- 50Hz or 60Hz environmental noise
- Ground and Supply Current Return Paths

Use continuous Ground Plane and  
Filter Supply traces

- **Signal Paths**


- Digital Switching noise
- Noise Generated by Previous Device

Use Analog Filters

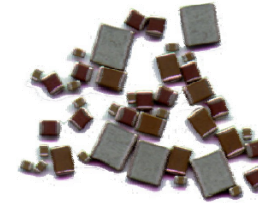
# Bypass Capacitor Types

- **Filters Noise at High Frequency**

- Ceramic - Small Case size, Inexpensive, Good Stability, Low Inductance





- NPO
- X7R

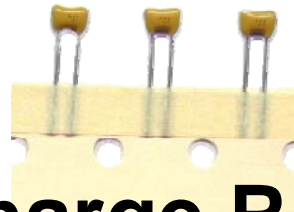


- **Acts as a Charge Reservoir for Fast Changes**

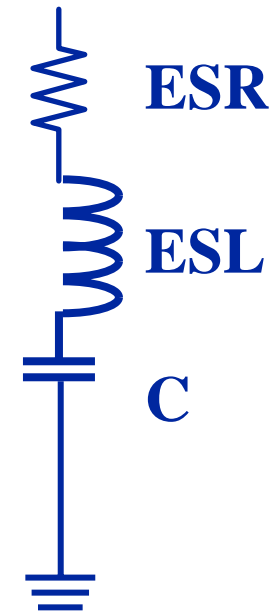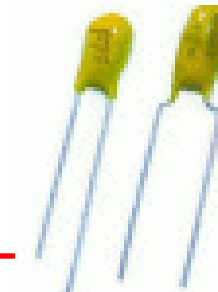- Tantalum Electrolytic - Small size, Large Values, Medium Inductance




# Response of Bypass Capacitors

## 12-bit A/D Converter

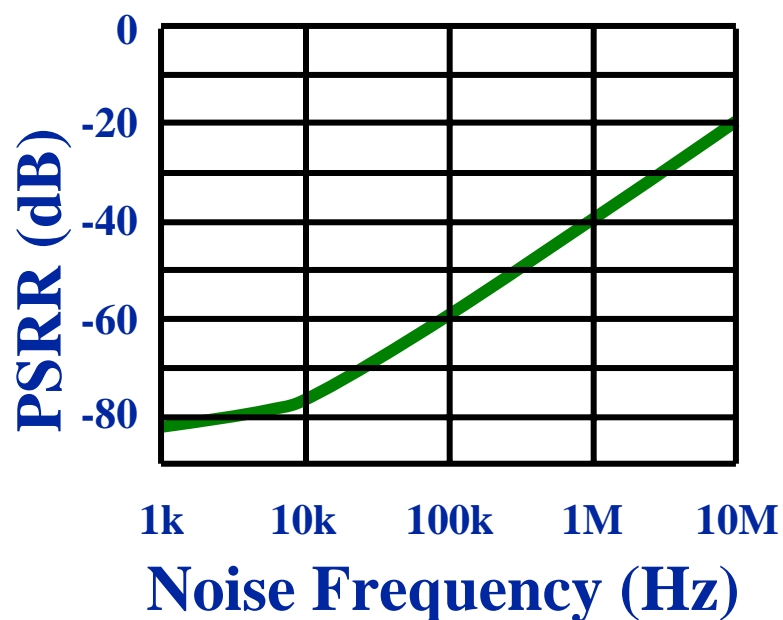


## Capacitor Response

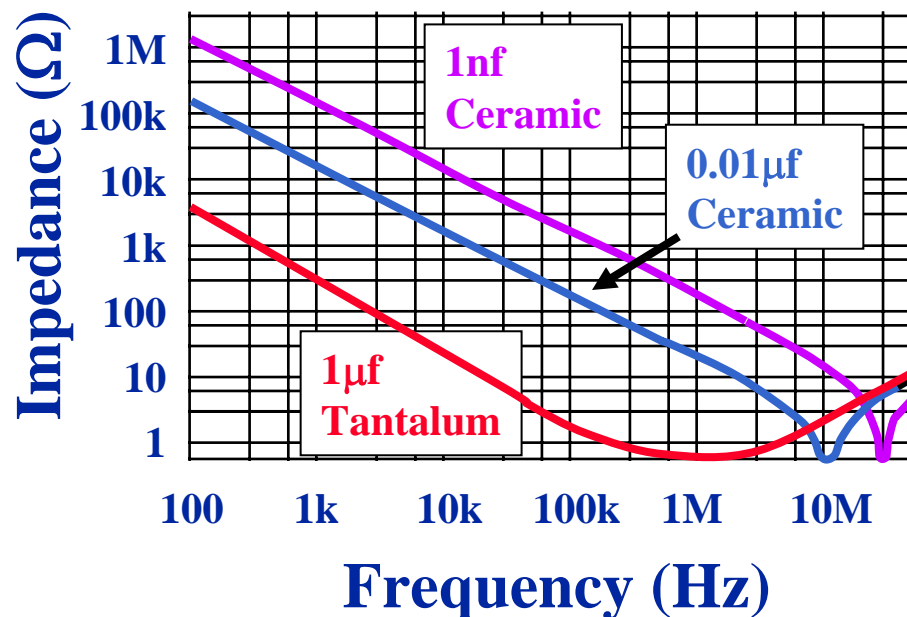

- **Assume:** Supply = 5V ± 20mV (all white noise)
  - To bring the noise to ± 1/4 LSB (± 0.61mV)
  - $PSRR = 20 \log_{10}(\delta\text{Signal} / \delta V_{dd}) < -30.3\text{dB}$
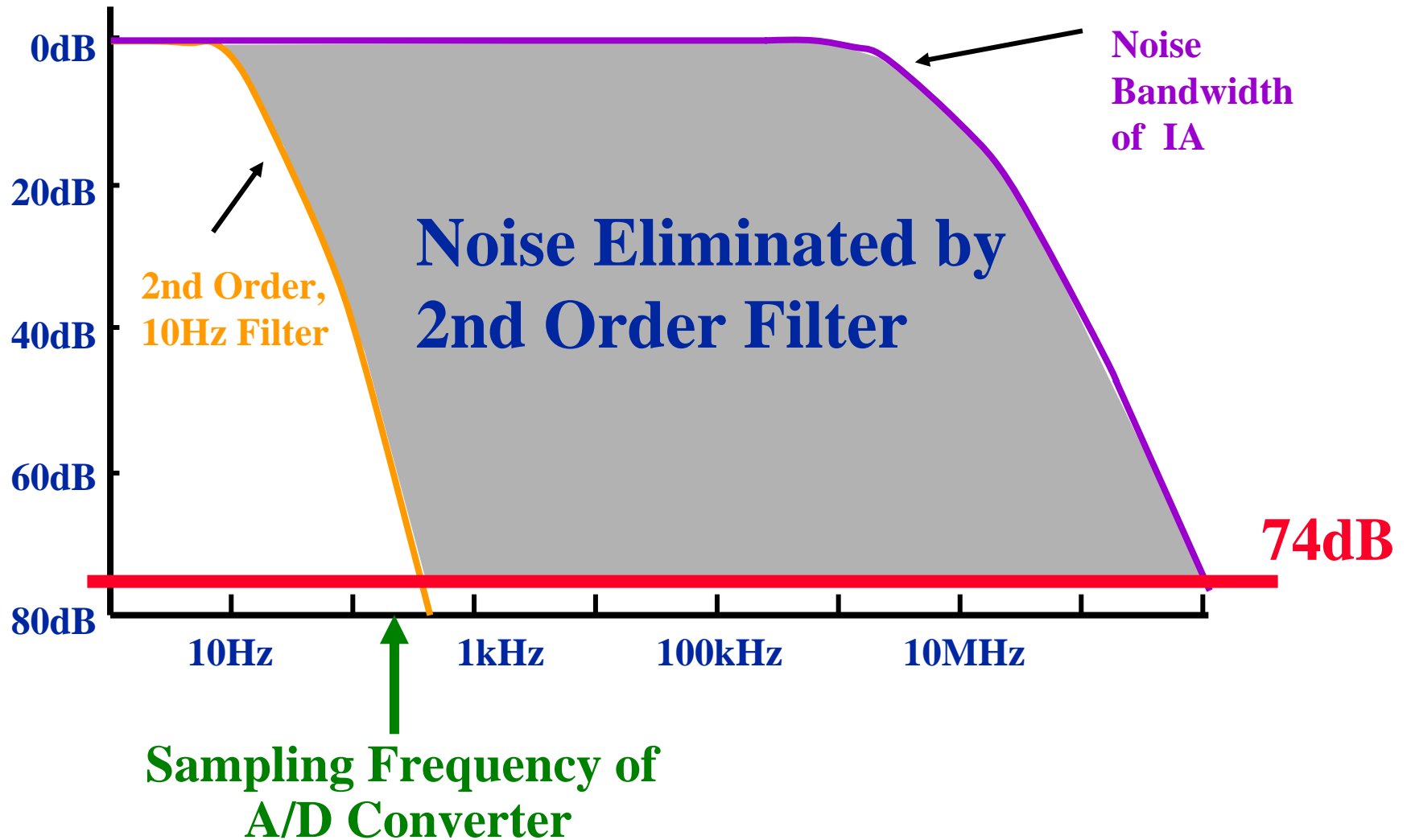
# Noise Reduction with Low Pass Analog Filter



# Application Circuit

## 12-bit Accurate Circuit Components


Low-pass filter

$$R_5 = 27.4\text{k}\Omega, R_6 = 196\text{k}\Omega, C_1 = 100\text{nF}, C_2 = 470\text{nF}$$


Bypass Capacitors

Ground Plane

MCP3201 = 12-bit, A/D SAR Converter

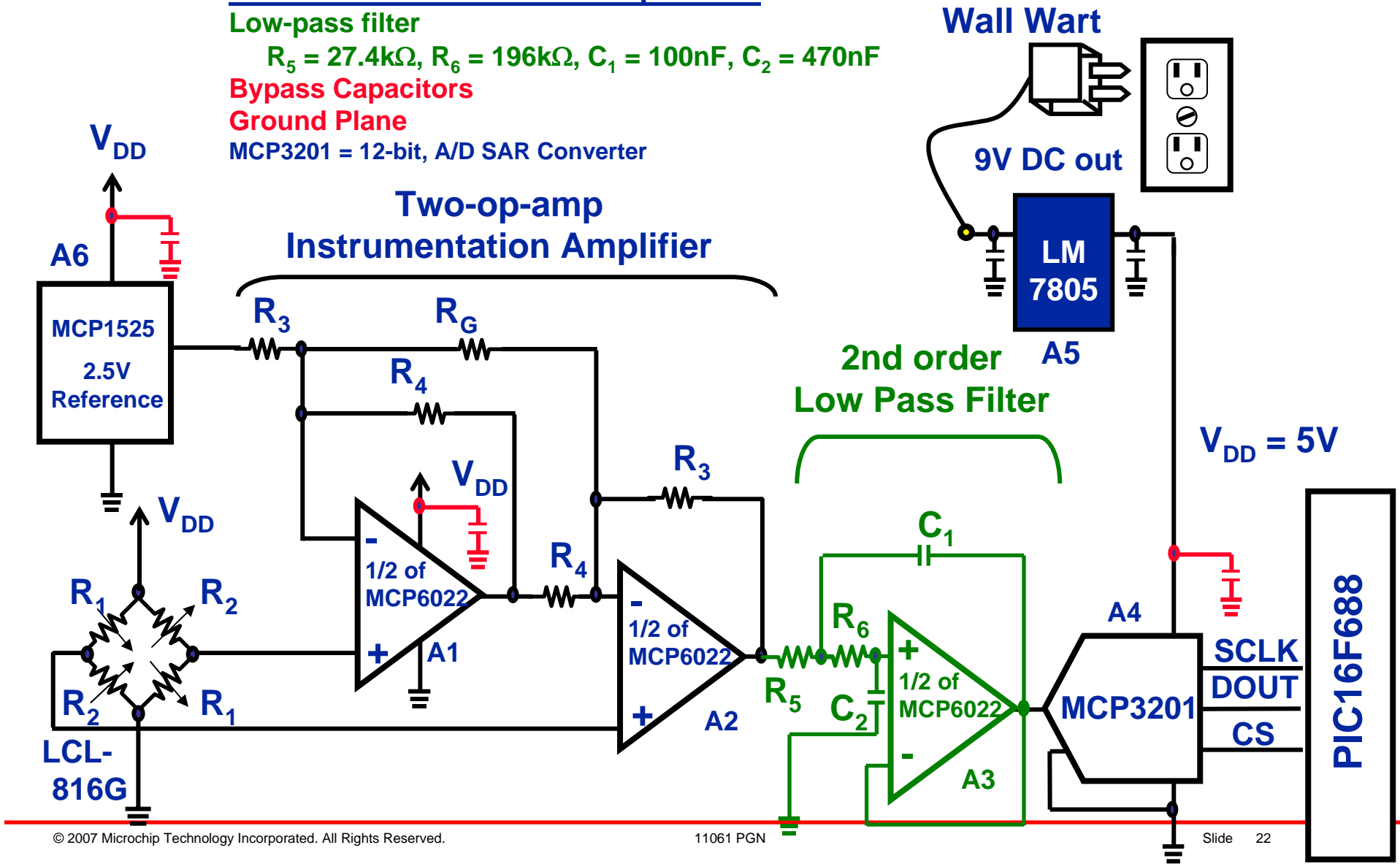


# Application Board #3 (top side)

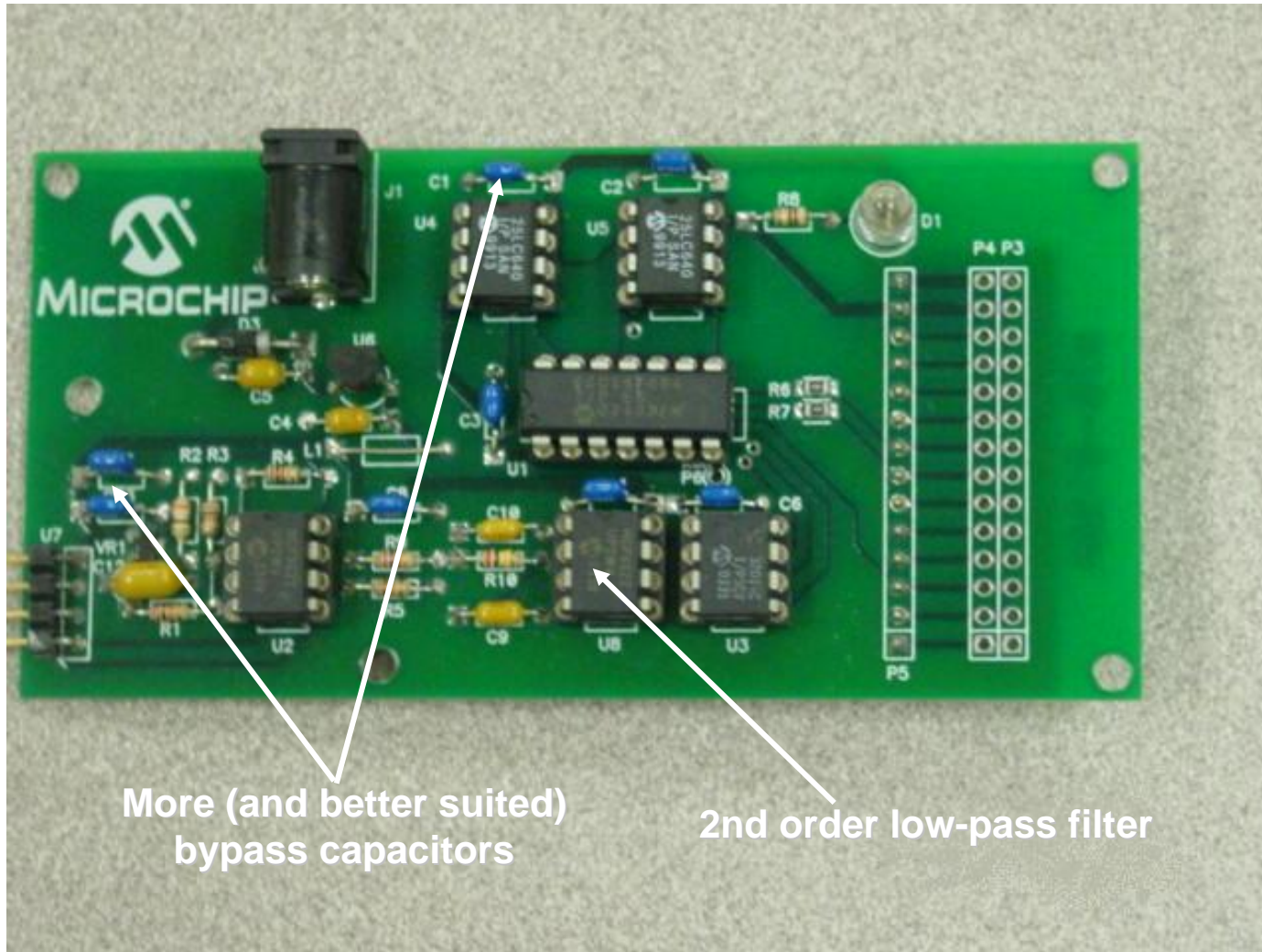



# Application Board #3 (bottom side)

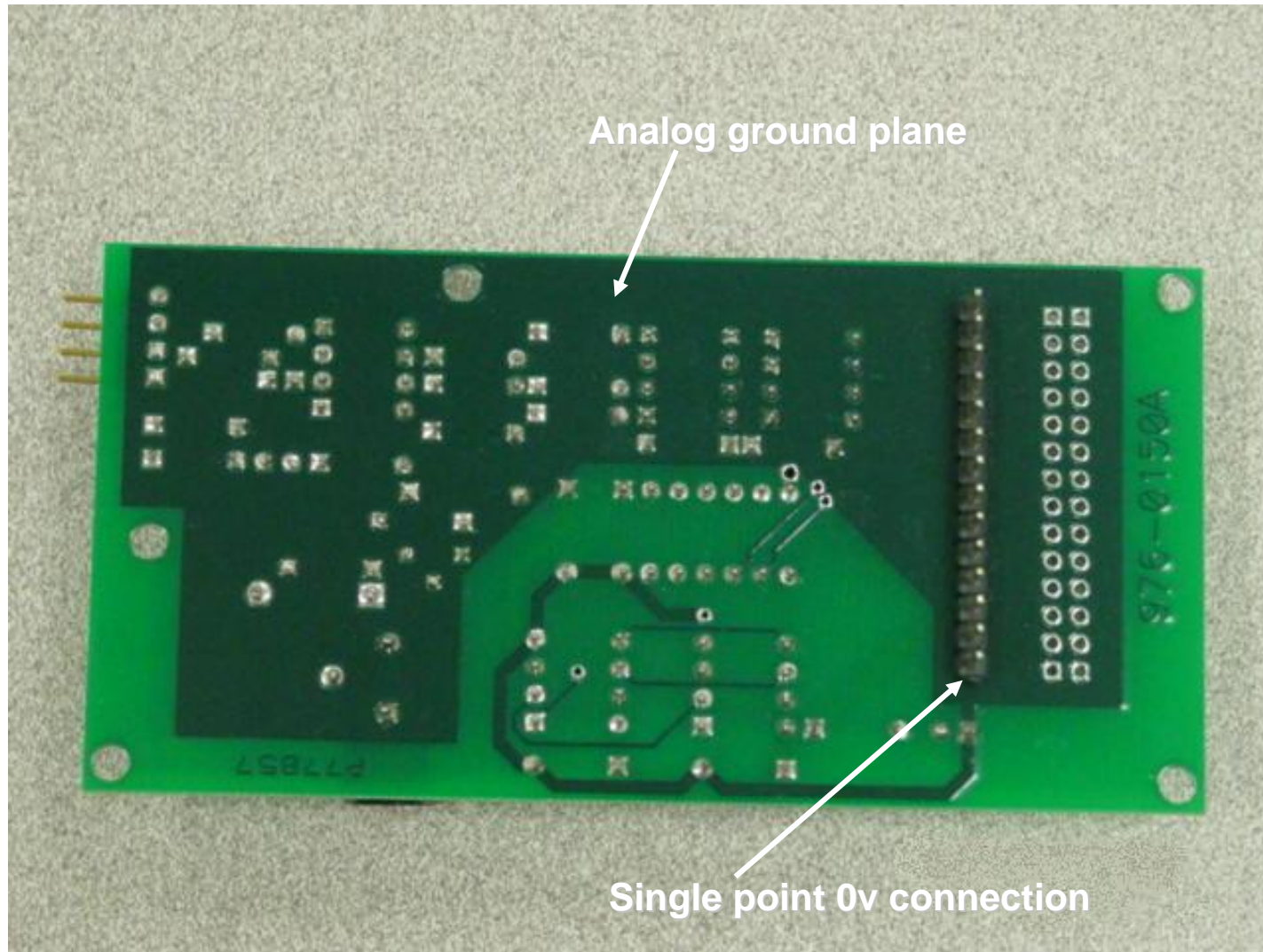




# App Board #3 Test Results

**Code Width  
of Noise = 1**

**(total samples = 1024)**

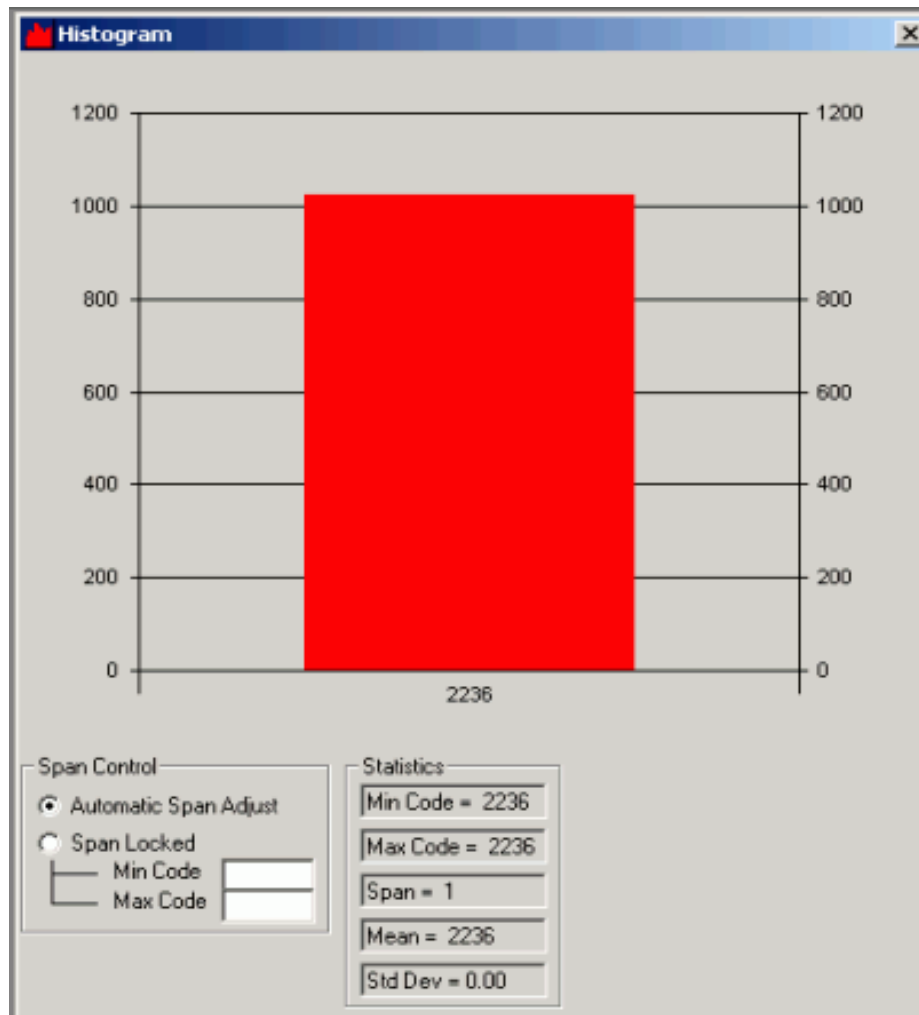

# Digital Design Agenda


- **First Pass**

- Digital Section
- Typical design rules and Layout
- Resulting performance


- **Second Pass**

- Identify sources of noise
- Identify noise pathways
- Develop VDD and VSS distribution plan
- New Layout and Resulting Performance

# Digital Section Block Diagram

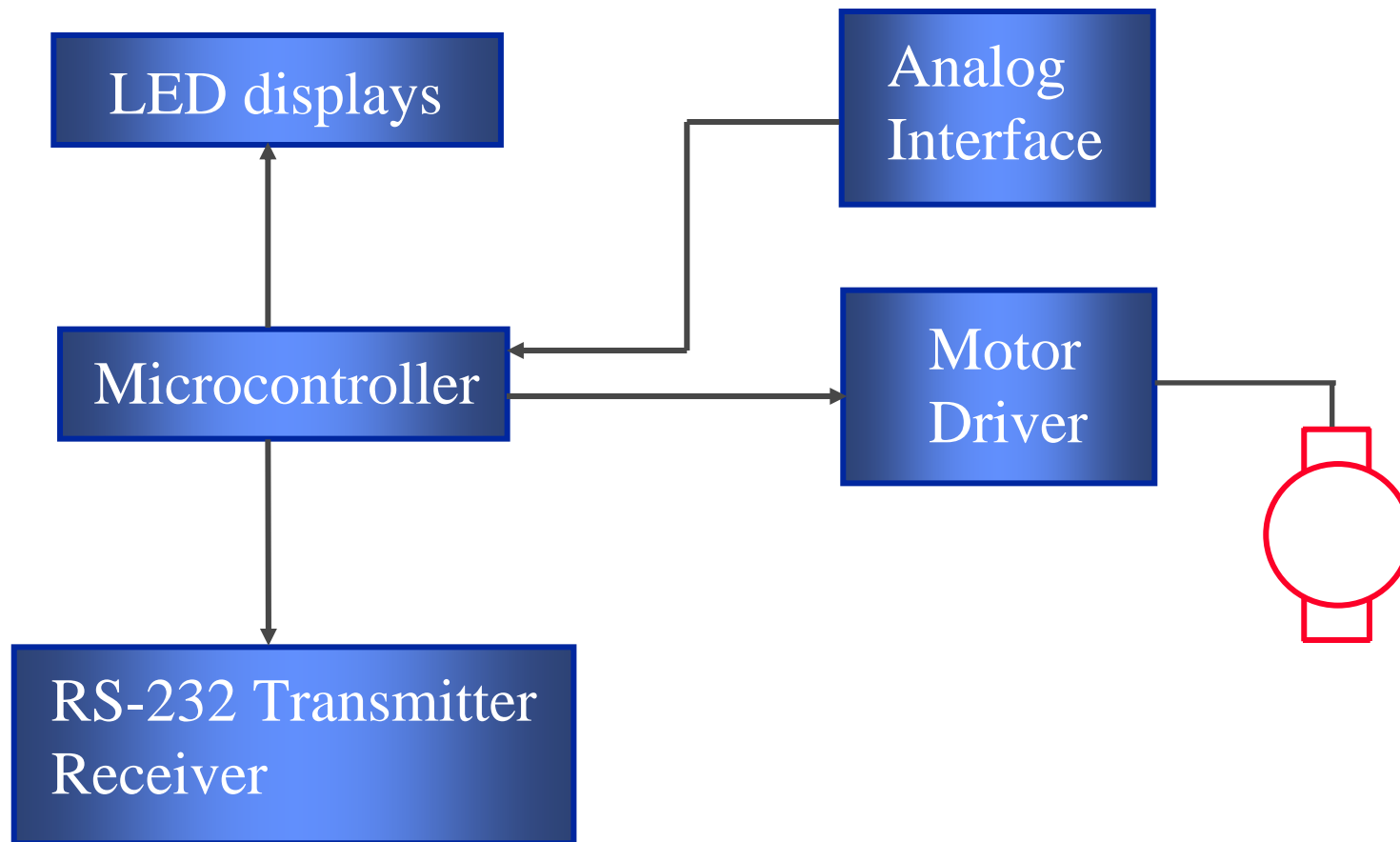

# Digital Section Schematic

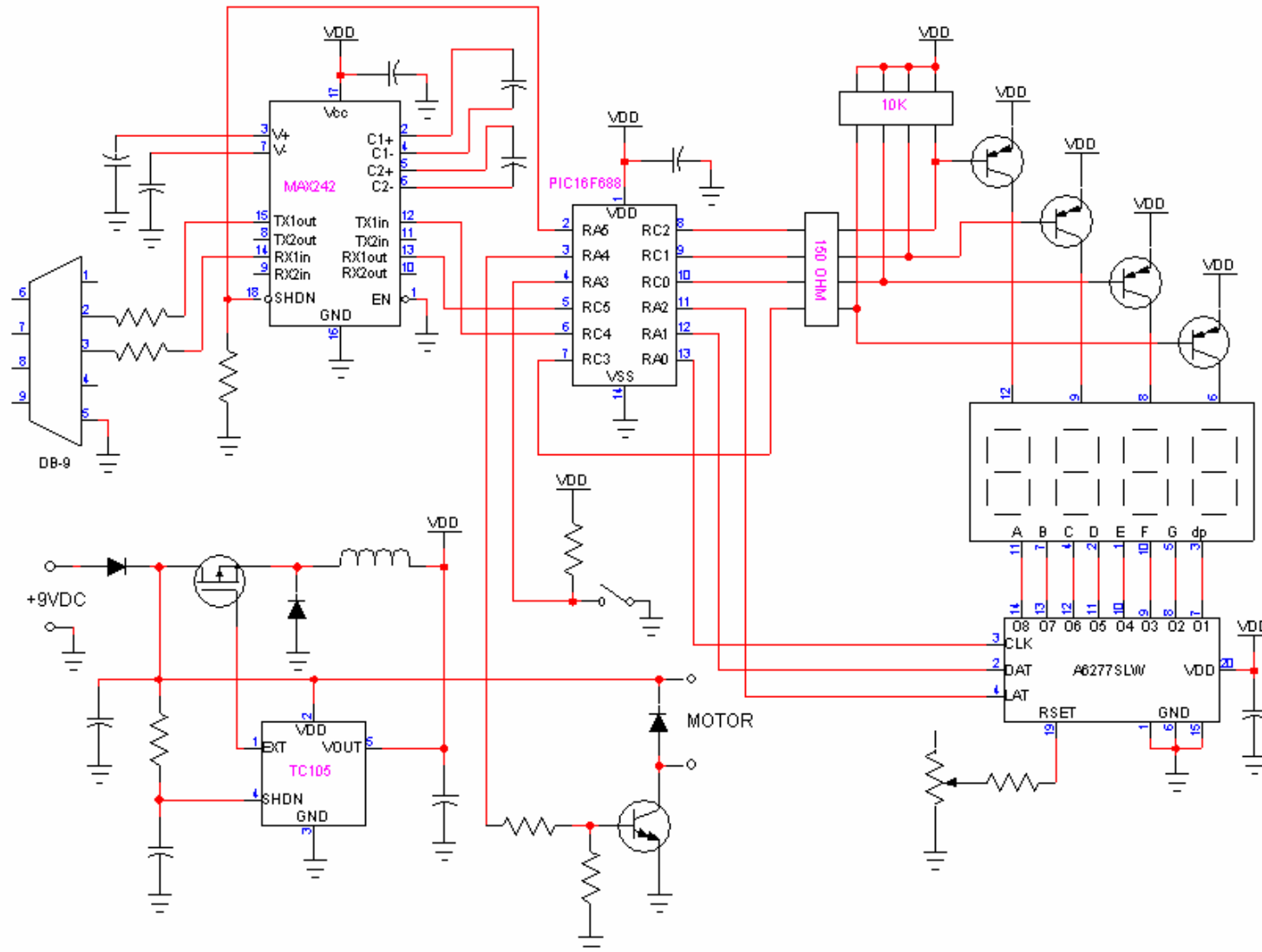

# Design Rules of Thumb


- **Digital Design Rules**

- Use bypass capacitors for each IC
- Use a back-EMF diode on the motor drive
- DON'T Modify the analog circuit


- **Board Layout Rules**

- Keep bypass capacitors near IC
- Keep Power and Ground traces short
- Avoid cuts in the Ground Plane
- Make Power and Ground traces larger

# First Pass Combined Layout

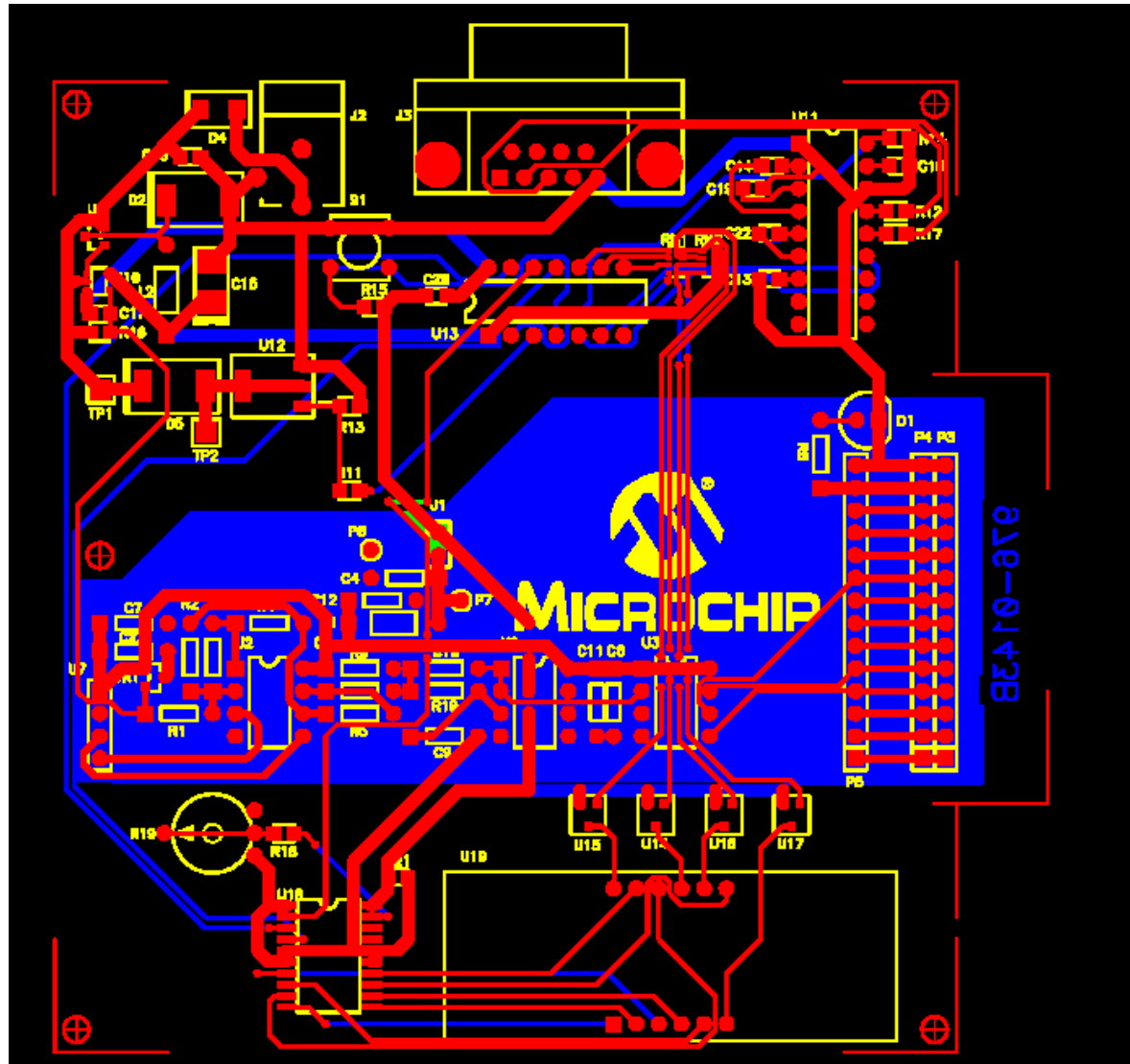


# Application Board #4 (top side)

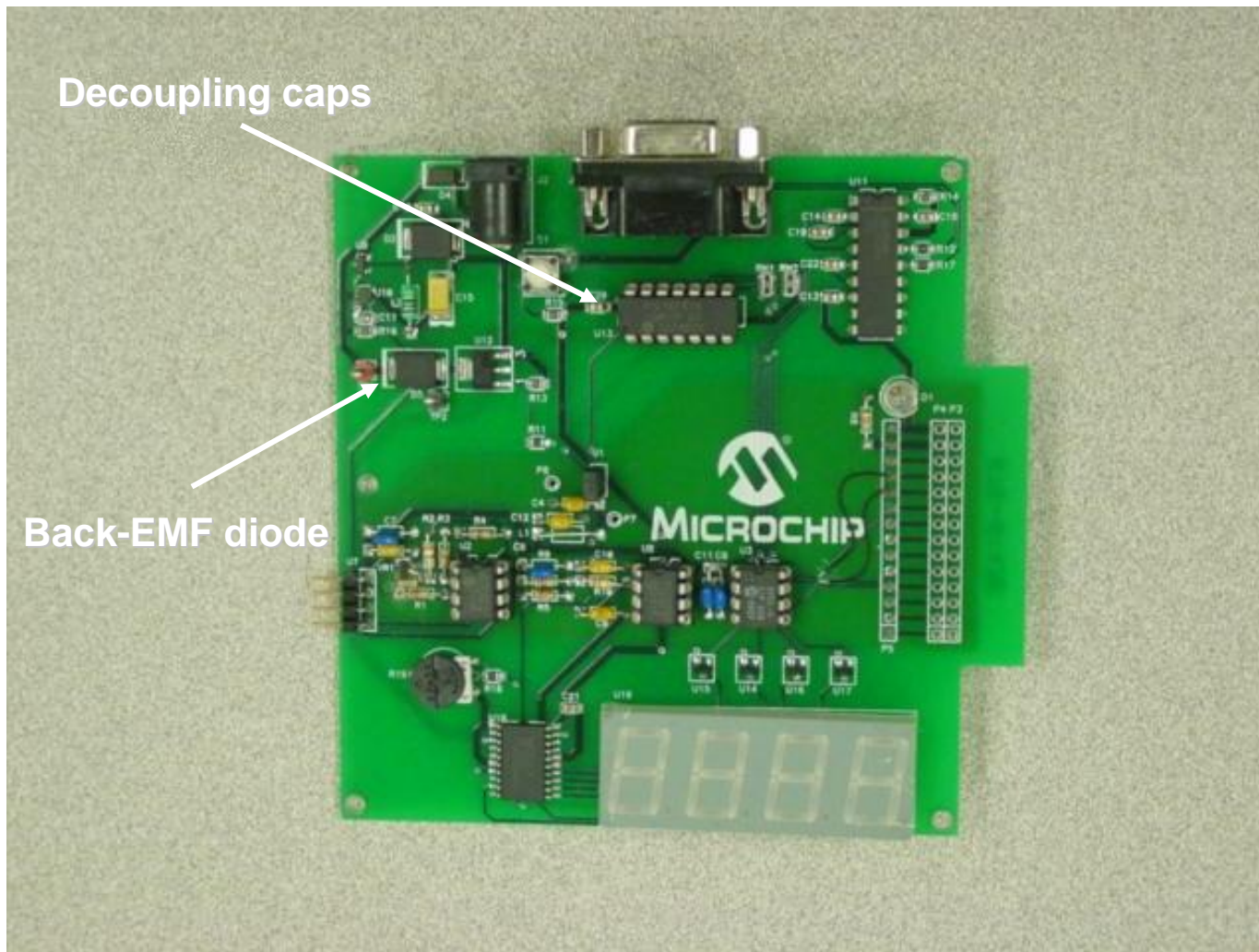




# Application Board #4 (bottom side)

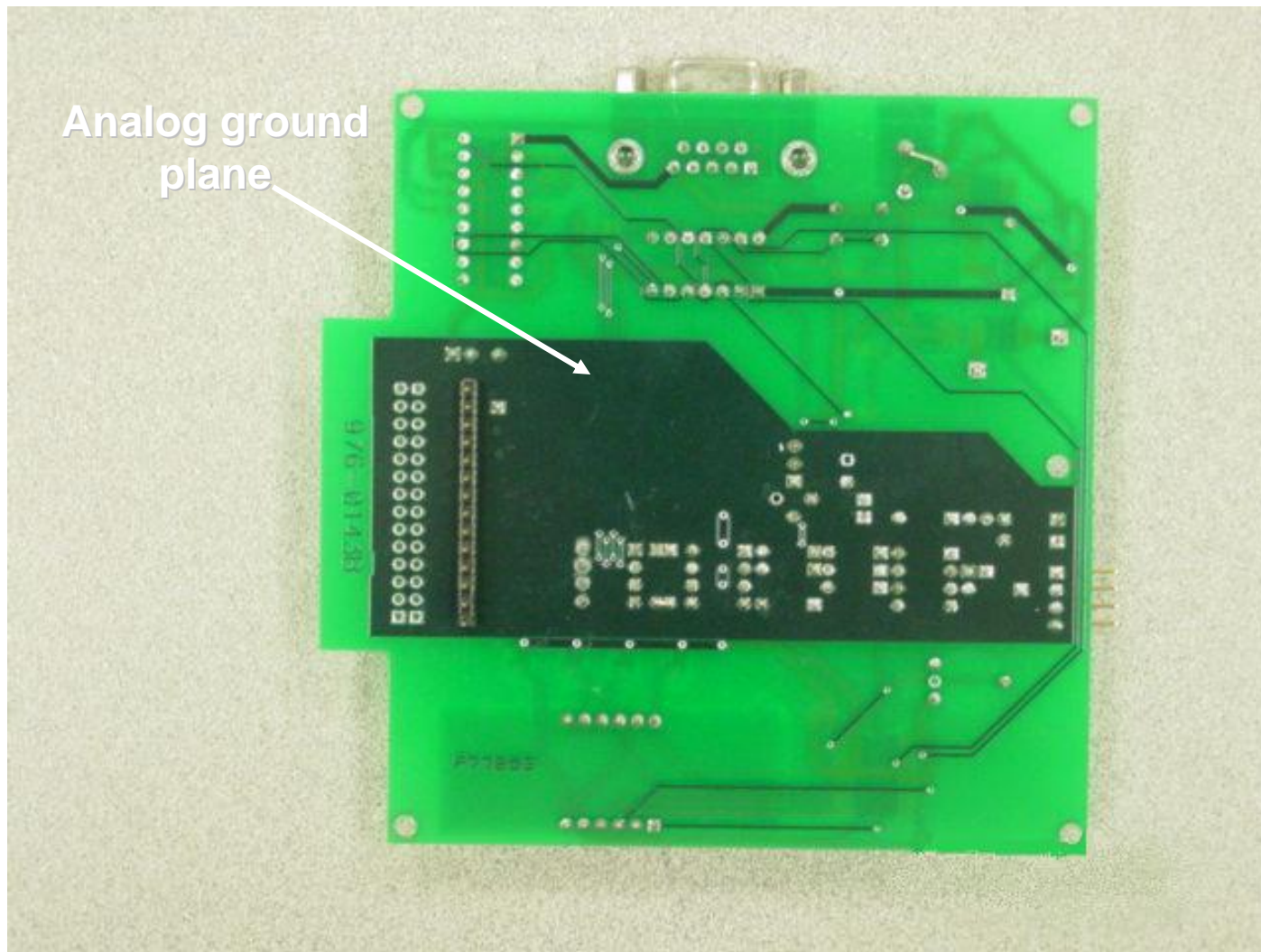


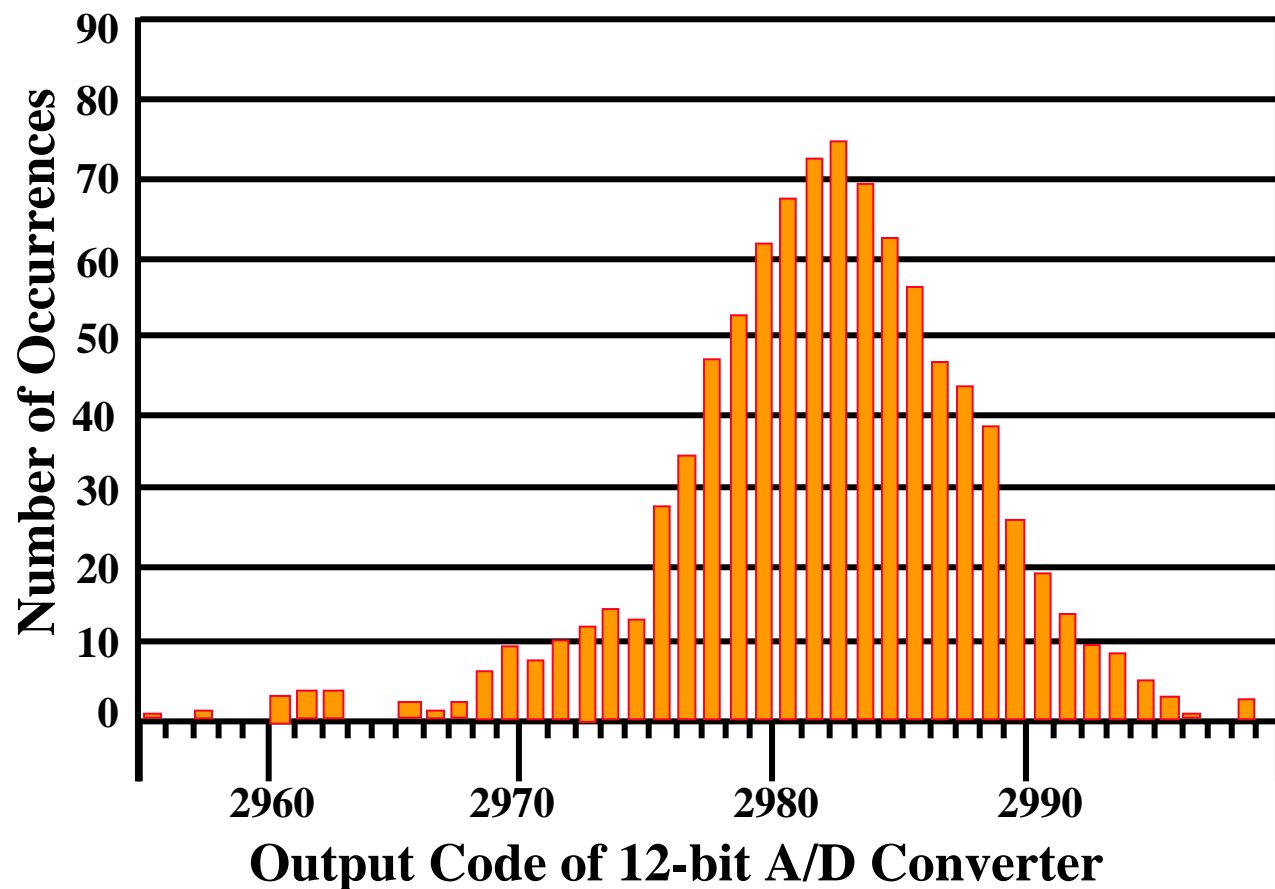
# Combined Analog/Digital Test-Board Results



**Code Width  
of Noise = 44**

**(total samples = 1024)**

# DENIAL!!

**I didn't touch the analog section,  
IT IS NOT MY FAULT!**

# Second Pass

- **A More Holistic Approach to Power Ground and Noise**
  - Identify the noise sources
  - Identify the noise pathways
  - Develop a Power and Ground distribution plan that:
    - **Isolates the noise sources**
    - **Restricts the noise pathways**
    - **Considers the circuit as a whole**

# Identify the Noise Sources


- **Internal noise sources**

- Switching noise generated by fast rise time signals
- Switching noise generated by high voltage/current switching

- **External noise sources**

- Externally generated Electro-Magnetic Interference or EMI
- May be radiated or conducted into the application

# Identify the Noise Sources

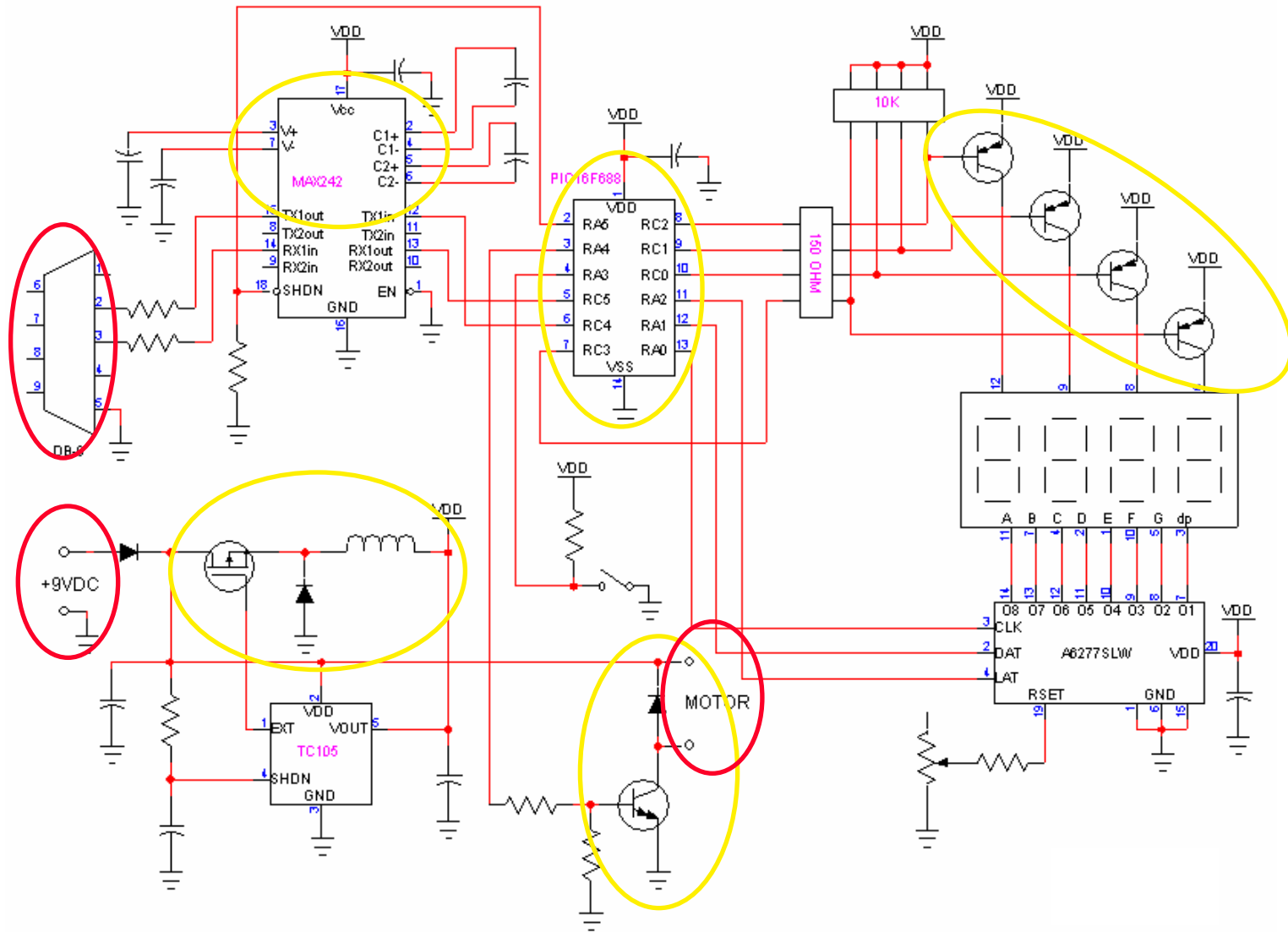


# Identifying Noise Pathways

- **Pathways for Conducted noise**
  - Power and Ground currents interacting with the trace resistance and inductance
  - External wires can transport noise
- **Pathways for Radiated noise**
  - Capacitively coupled from fast rise time signals in close proximity
  - Magnetically coupled from high current signals in close proximity, or through a ferrous material
  - Traces acting as Antennas for incoming RFI

# The Physics of the Problem

# PCB Crosstalk

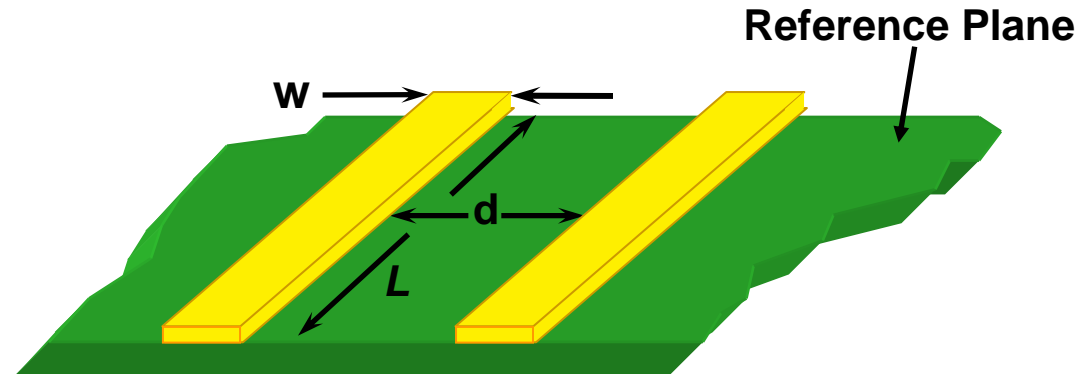

- **Reduce crosstalk noise by**

- ↑  $d$  (distance)
- ↓  $L$  (parallel length)
- ↓  $t_r$  (rise, fall times)
- ↓ Characteristic impedance

- **Reduce noise by**

~~Parallel~~

- **Keep  $R_{IN}$  &  $R_{OUT}$  Small**



# PCB Inductance

- Significant source of ground noise

$$V_{\text{noise}} = L \frac{di}{dt} \text{ volts}$$


- For a trace above a ground plane  
 $L = 0.005 \ln(2\pi H/W) \text{ uH/in}$

- For a current loop (e.g. power & ground return)  
 $L_t = L_{\text{pwr}} + L_{\text{gnd}} - 2M$  (M=mutual inductance)

- Reduce Noise by


↓ H (height above return path)

↑ W (width of trace)

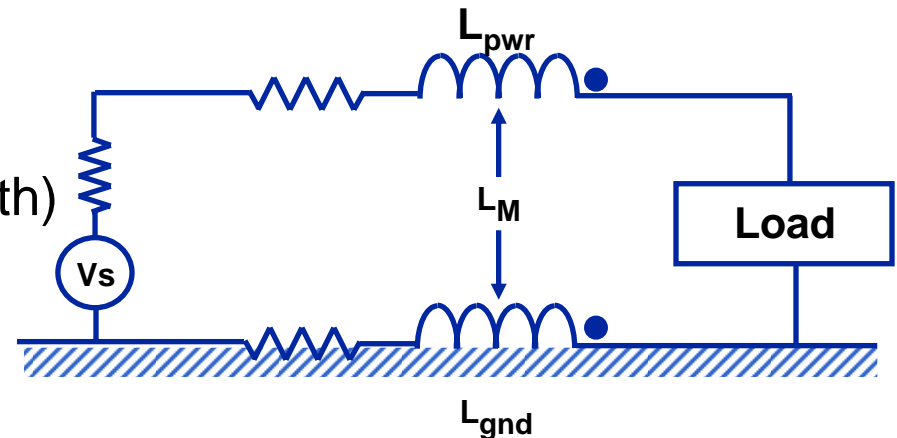

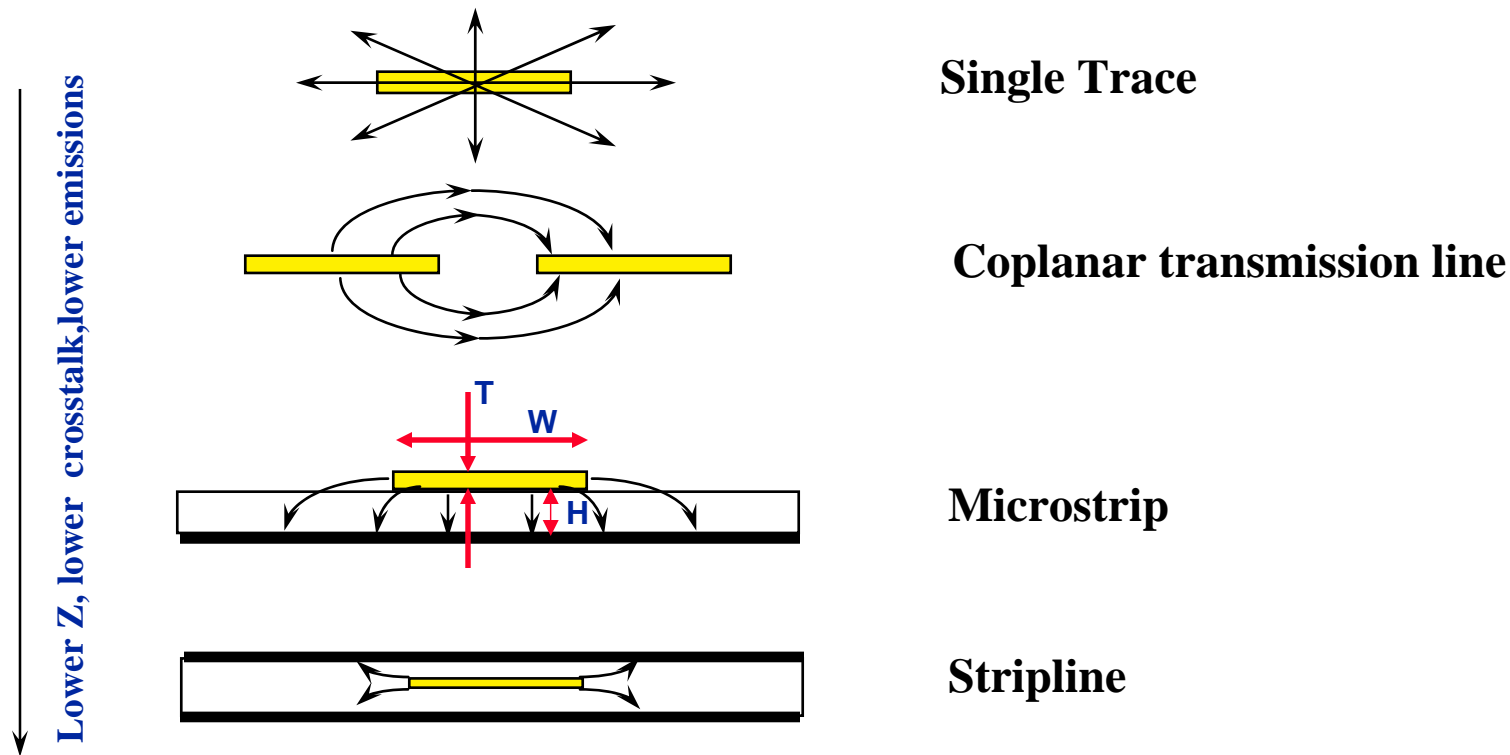
# PCB Trace Impedance

- Avoid creating traces without a clearly defined return path (especially for clock signals)
- Lower  $Z_0$  = Less crosstalk, lower RF emissions


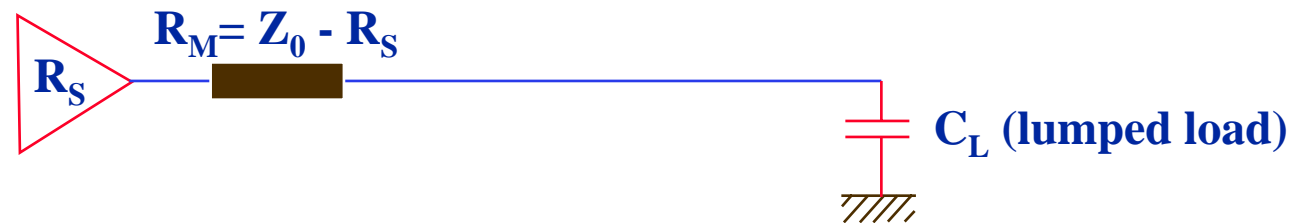
# Reflections & Ringing

- **Traces may be unterminated if**
  - $L(\text{cm}) < 9 * t_r (\text{ns})$   
 [Estimate based on microstrip topology and 0.36ns/cm (FR-4)]
- **Terminated lines: series R is typically the most appropriate (but will introduce delay,  $T_{pd}$ )**




- **$Z_0$  varies with  $T$ ,  $W$  and  $H$ .  $T_{pd}$  varies with  $\epsilon_r$** 
  - For  $W \gg H$ ,  $Z_0 = \frac{377 * H}{\sqrt{\epsilon_r} * W}$  ohms
  - $T_{pd} = 33.37 \sqrt{0.475 \epsilon_r + 0.67}$  ps/cm
  - See references for more precise  $Z_0$  and  $T_{pd}$  calculation

# PCB Trace Resistance

$$R = \frac{L \cdot \rho}{W \cdot T} \quad \text{ohms}$$

where  $\rho$  = resistivity

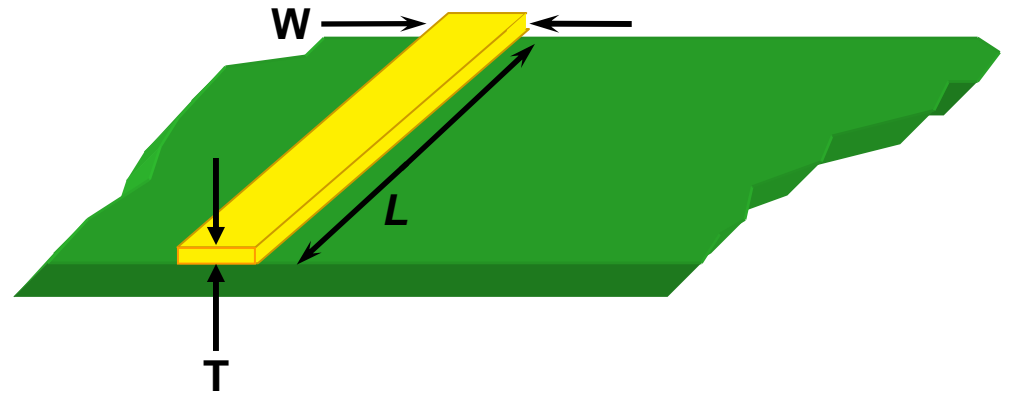

$$V_{\text{drop}} = I R \text{ amps}$$

- **Reduce Noise by**
  - ↑  $W$  (width of trace)
  - ↓  $L$  (length of trace)
  - ↑  $T$  (thickness of trace)

# The Usual Suspects

# Ground Impedance Effects

- **Common-impedance coupling**
  - Can introduce digital noise into sensitive analog or interface subsystems
  - Can cause RF noise to couple onto external ports
- **Ground loops**
  - Source of RF emissions if the circulating current has a significant HF component
  - Can create havoc with partitioned interface circuitry
  - Can introduce line AC noise into low-level analog circuitry
- **Resonance**
  - Ground bounce can impact signal integrity of bus structures
  - Multi-point ground resonance can induce sufficient ground movement as to cause systems to fail, especially during susceptibility testing

# Conducted Noise Pathway: Ground

- **Pathway: Ground, carries return currents and provides a reference voltage,**
  - Fast rise time currents react with trace inductance to generate noise voltages
  - High currents react with trace resistance to generate noise voltages

# Conducted Noise

## Corrective Action: Ground

- **Minimize AC and DC impedances.**
  - Make all grounds as short and wide as possible
  - Ground planes are better than traces
- **Isolate noisy Ground returns**
  - No fast currents through sensitive grounds or ground planes
  - No high current in sensitive grounds or ground planes



# Conducted Noise Pathway: Power

- **Pathway: Power, the source of operating current**
  - Fast rise time currents react with trace inductance to generate noise
  - High currents react with trace resistance to generate noise

# Conducted Noise

## Corrective Action: Power I

- **Minimize Impedance**

- Make Power traces as wide as possible
- Keep leads to bypass capacitors short to limit inductive responses to switching (self resonance effects)
- Use low ESR bypass capacitors to limit resistive responses to switching

# Conducted Noise

## Corrective Action: Power II

- **Isolate noise sources using low pass filtering**
  - Isolate noisy circuits on their own power traces to create higher series impedances
  - Properly selected bypass capacitors to present a low shunt impedance
  - Together, trace inductance and bypass capacitors create a LP filter
  - Ferrite beads, inductors, and resistors can augment the lead inductance to lower the corner frequency of the low pass filter

# Radiated Noise

- **Pathway: Adjacent Traces**


- Adjacent traces can create unintended capacitors which can couple fast signals
- Adjacent traces can create unintended transformers which can couple high current signals

- **Corrective Action: Adjacent Traces**

- Both are minimized by increased distance
- Both are minimized by decreased common area
- Low impedance signals are less susceptible
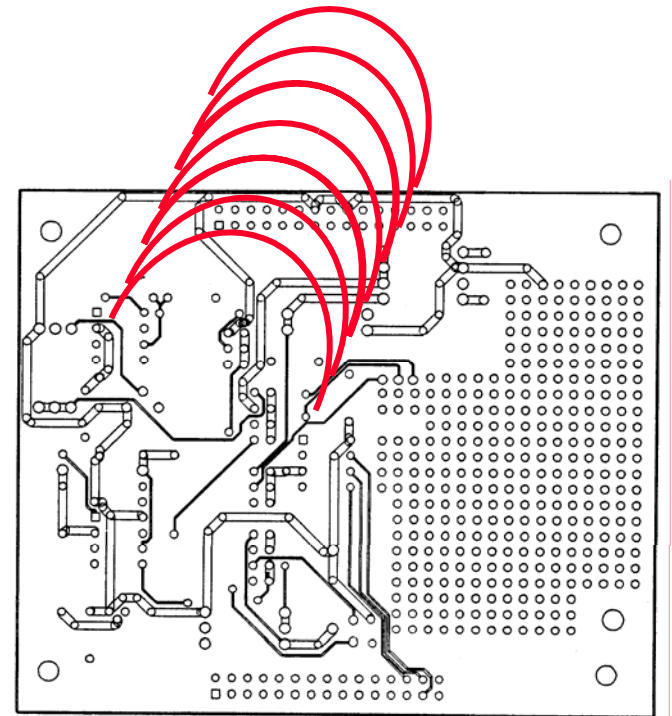
# Radiated Noise

- **Loops: Magnetic fields can couple locally and/or radiate**  
 $E \propto A I_L f^2 / \text{distance}$  (far field  $E/H=377\text{ohms}$ )  
*E increases at 40dB/decade*
- **Traces and wires can act as Antennae for noise**  
 $E \propto L I_{cm} f / \text{distance}$   
*E increases at 20dB/decade*
- **High frequency signals will radiate more if not terminated**
- **The Q Multiplier effect can generate high voltages in resonant circuits**




# Radiated Noise Corrective Action

- **Keep sensitive signal traces short**
  - Shield sensitive/noisy wires or long traces
- **Terminate signals resistively**
- **Minimize current loop areas**
  - Decouple as locally as possible
  - Minimize clock & oscillator return paths
  - Use ground planes as current return image plane
- **Use an RC or LC low pass filter on all signals entering the cabinet**
  - Filter to cabinet ground
    - Exterior for inputs, interior for outputs
- **Use low impedance drivers to transmit signals over long distances**
- **Match load impedance to source impedance**
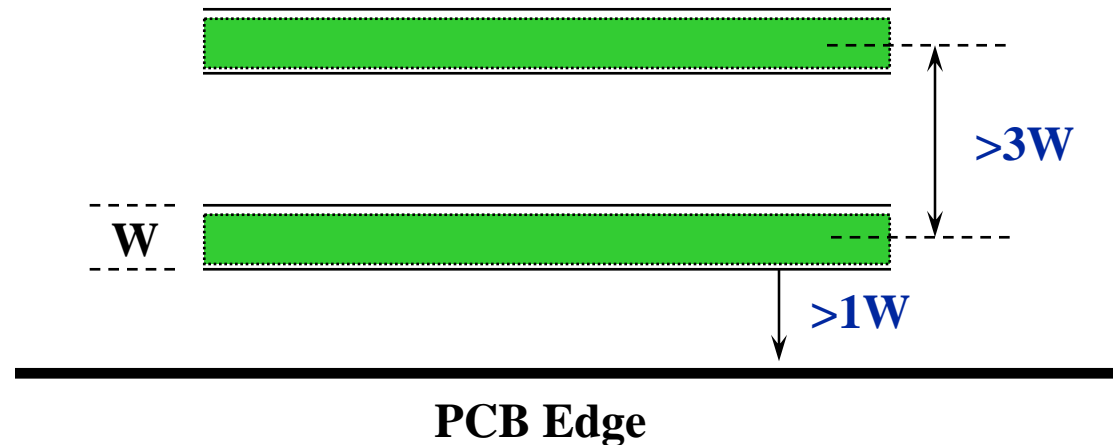
# The 3-W Rule

- Represents 70% flux boundary
- Removes the need for a guard trace in most cases
- Mandatory only for high threat signals (clocks, analog, reset, differential pairs)



# Creating a Power and Ground Distribution Plan




# Start with the Right Bypass Capacitor for Digital Sections

- Determine noise frequency

$$f_{\text{noise}} = 1 / (\pi * t_{\text{rise}}) \text{ or } t_{\text{rise}} = 1 / (\pi * f_{\text{noise}})$$

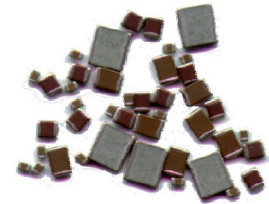[substitute  $t_{\text{fall}}$  if faster]



- Determine max ripple voltage  $V_{\text{RIPPLE}}$


- Approximate surge current

$$I_{\text{SURGE}} = I_{\text{AVE}} * f_{\text{noise}} / f_{\text{clk}}$$



- Calculate bypass capacitor value
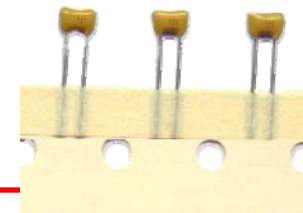
$$\begin{aligned} C_{\text{BYPASS}} &= \delta i * \delta t / \delta v \\ &= I_{\text{SURGE}} * t_{\text{rise}} / V_{\text{RIPPLE}} \\ &= \{ (I_{\text{AVE}} * f_{\text{noise}} / f_{\text{clk}}) * (1 / (\pi * f_{\text{noise}})) \} / V_{\text{RIPPLE}} \\ &= I_{\text{AVE}} / (\pi * f_{\text{clk}} * V_{\text{RIPPLE}}) \end{aligned}$$




# Creating a Power and Ground Distribution Strategy I

- Separate, classify and draw the various sections of the design, include the Supplies


- **Digital section**

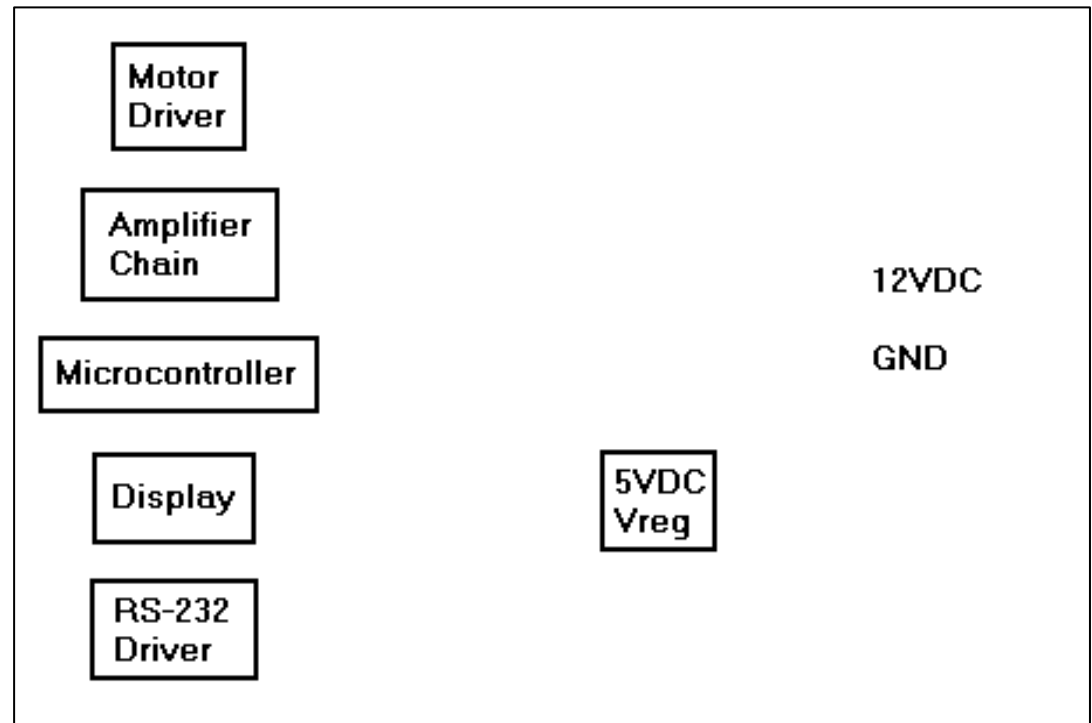- Clock is  $<5\text{MHz}$  &  $t_{r/f} > 5\text{ns}$  so single point ground OK
- Would require its own digital ground plane if  $>5\text{MHz}$ ,  $<5\text{ns}$



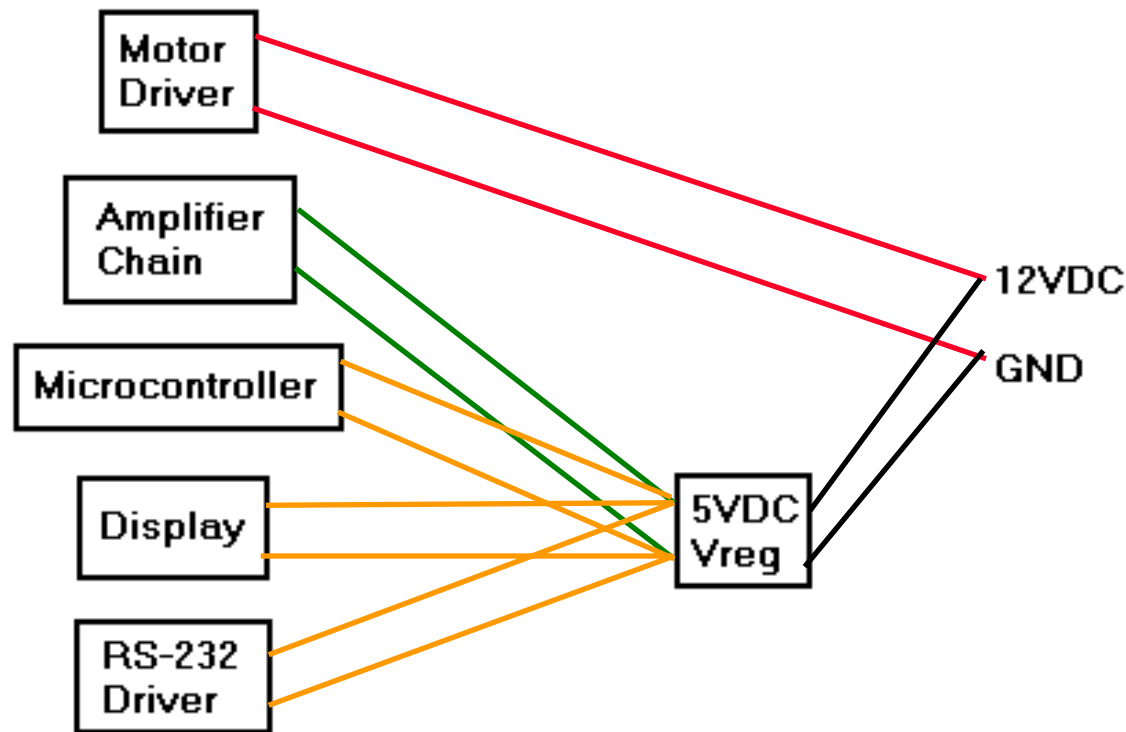
# Mapping out the plan

- Draw the sections of the design, and add the connections


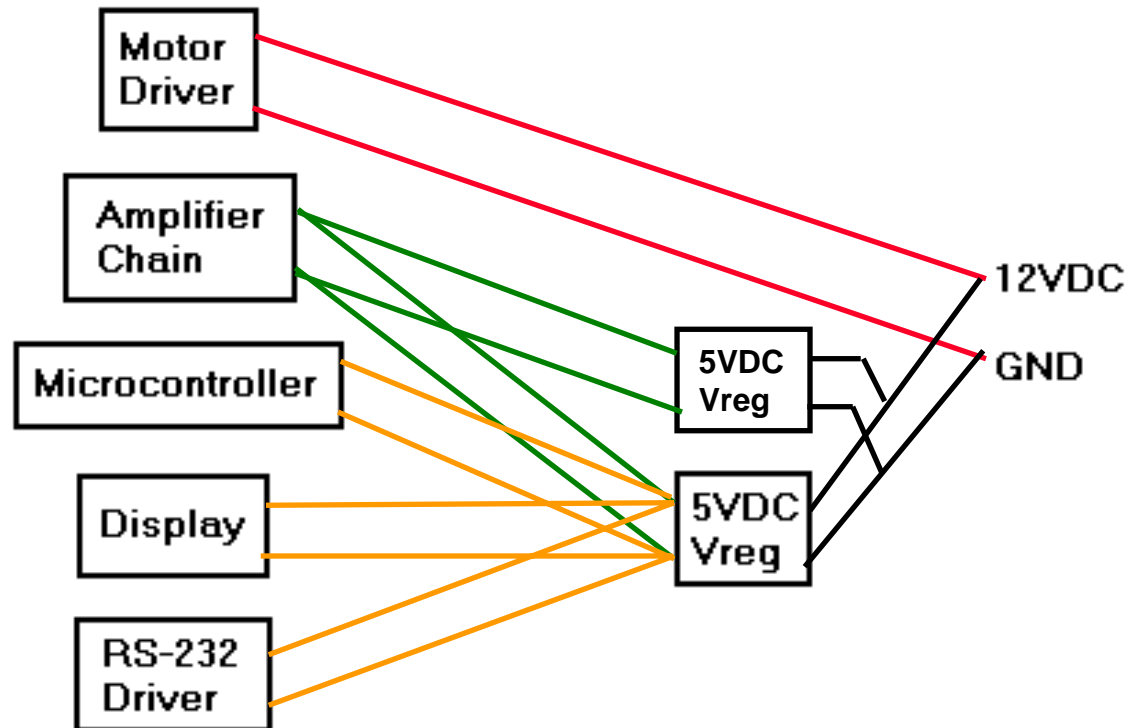
# Revising the plan


- Use routing to maximize isolation between noisy and sensitive blocks, while keeping runs short




# Re-layout the Board

- **Layout the board using the plan**
  - Think about isolation when placing each section
  - Think about how to route power and ground for each section
  - Remember to isolate sensitive signals from fast and high current signals
  - Remember which traces have to be wide
  - Remember which traces have to be short and wide

# Placement, Power and Ground

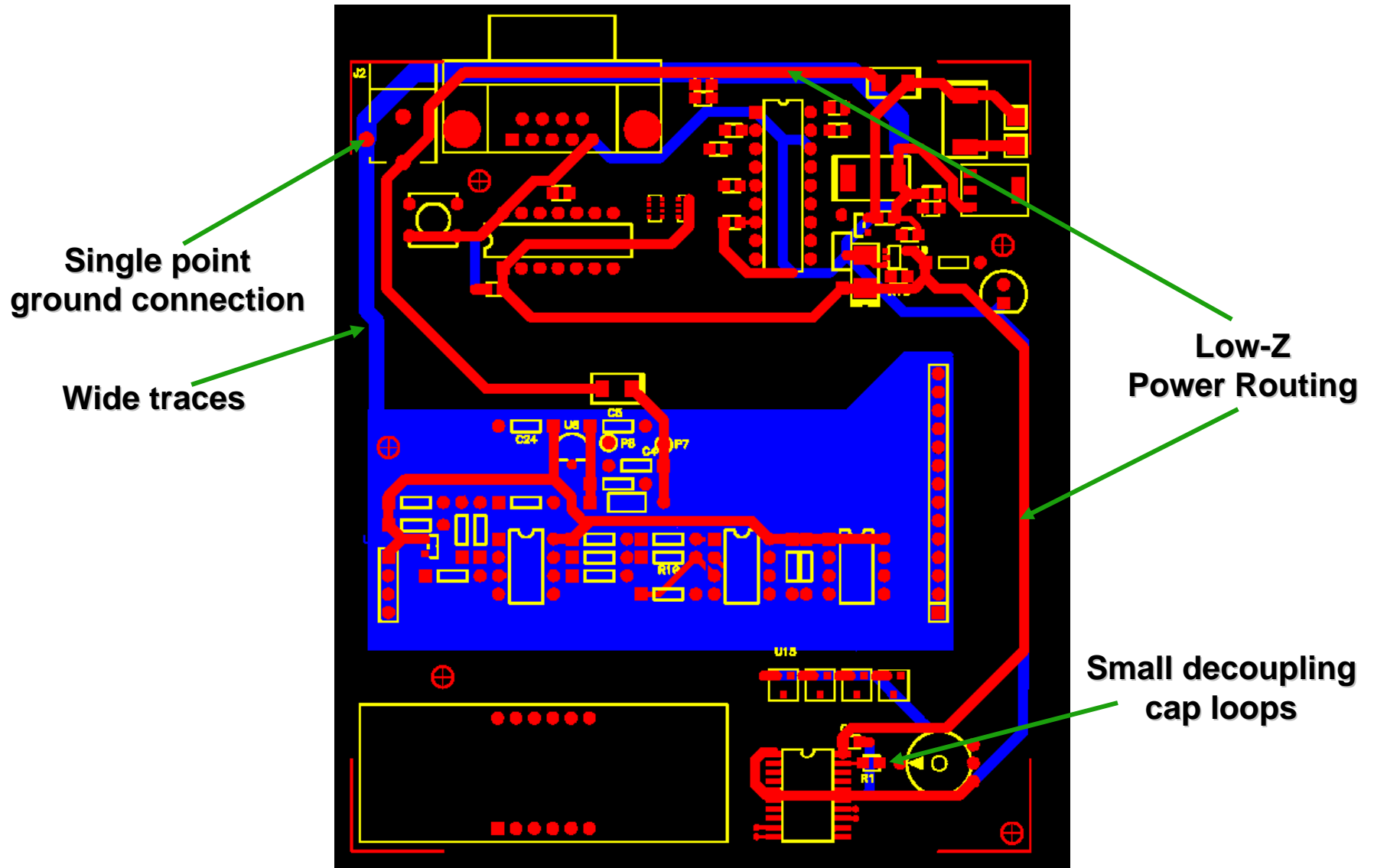


# Complete Board Layout

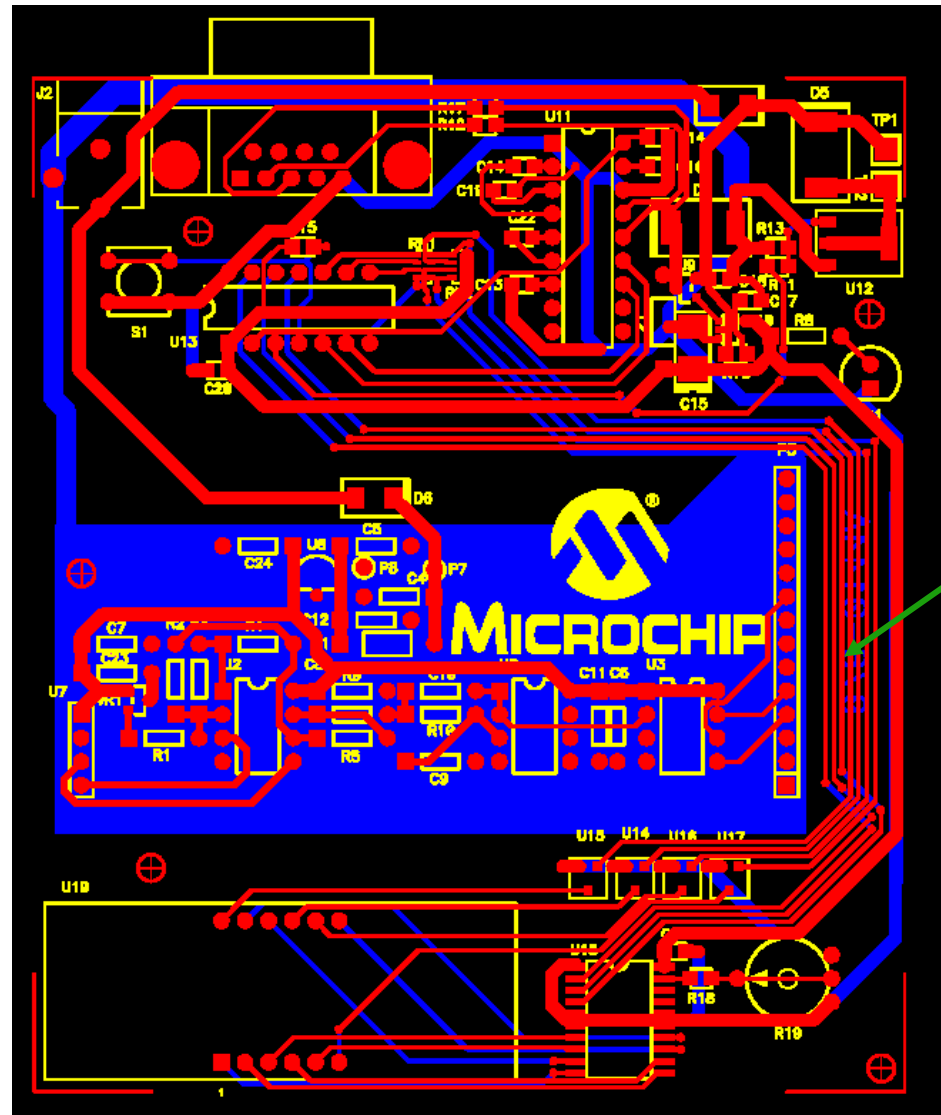


Re-route digital signals around analog area

# Application Board #5 (top side)

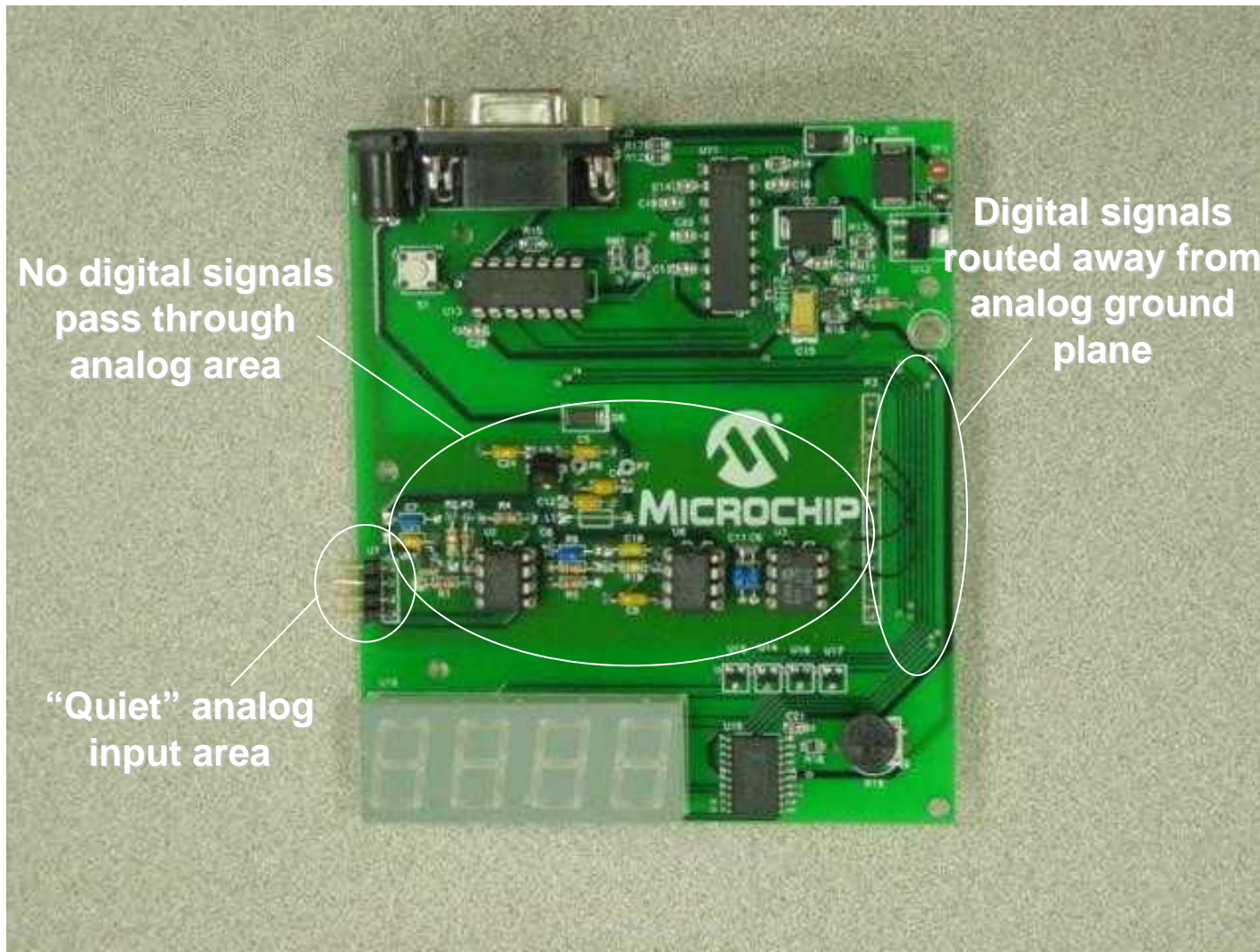




# Application Board #5 (bottom side)

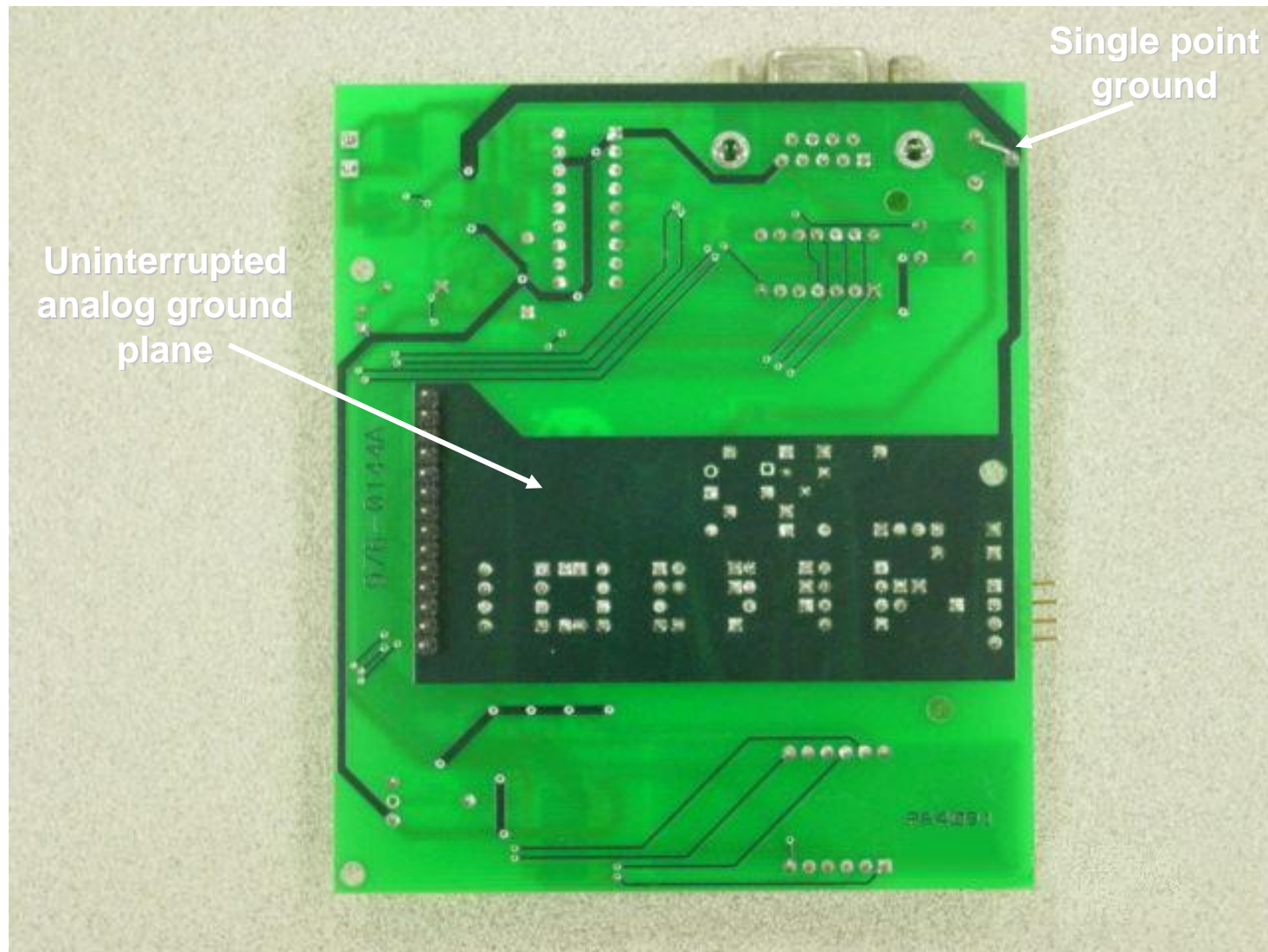

# New Composite Board Test Results

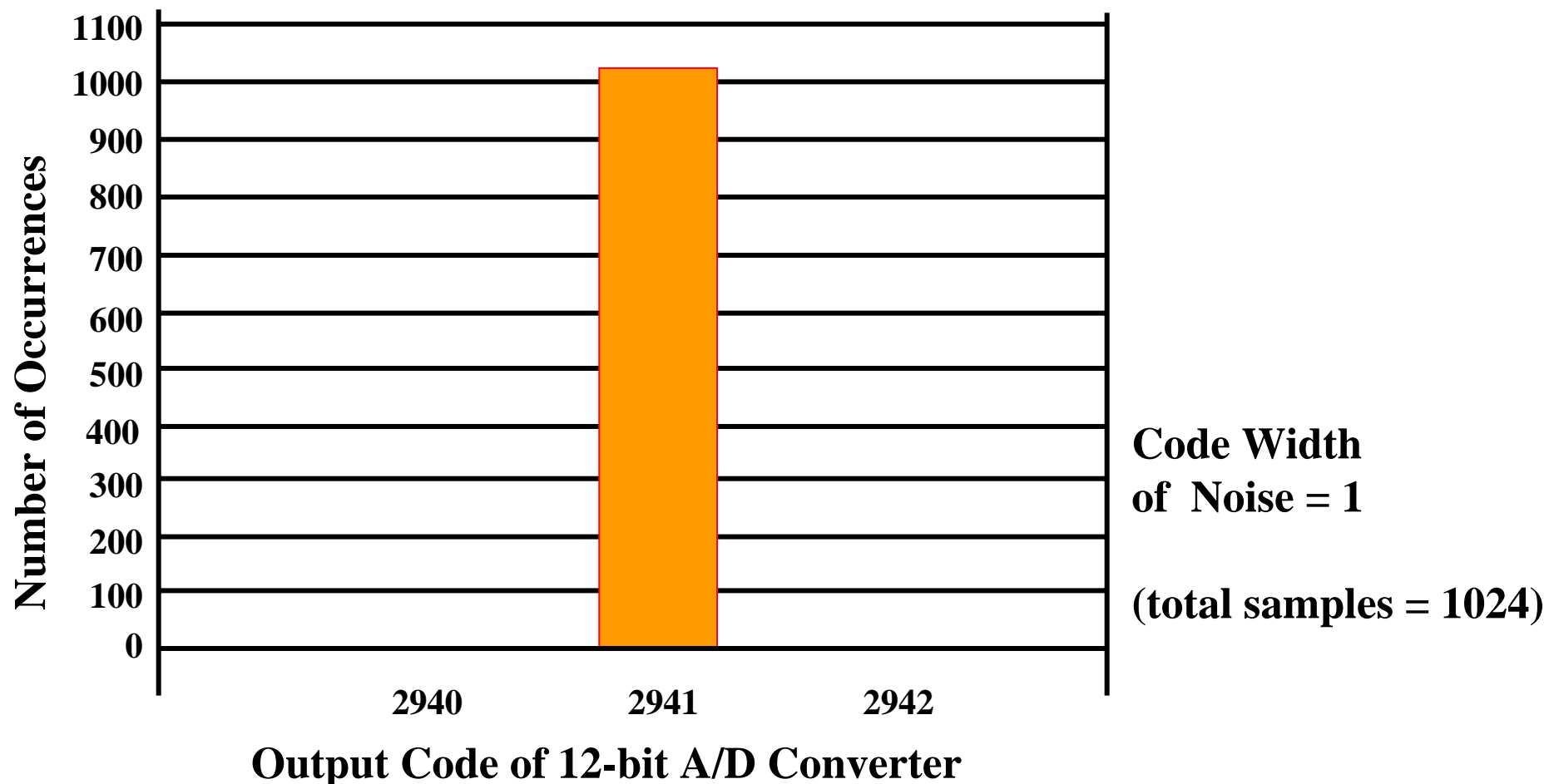

# Summary

- **Use low-noise analog components**
- **Use an uninterrupted ground plane**
  - Separate digital & analog planes using a ‘moat’
- **Filter the ADC with an analog low-pass filter**
- **By-pass all devices properly**
- **Filter your power supply properly**
- **Develop a power and ground plan for the whole circuit**
- **Isolate noisy sections**
- **Minimize noise pathways**

# Additional Noise Reduction Techniques

- **Using software to create quiet times for conversions**
- **Move switching power supply inputs to unregulated supplies**
- **Use separate analog and digital voltage regulators**
- **Use two or more bypass capacitors in parallel to extend their frequency range**
  - But be aware of double resonance effects

# References

## ● Reference Books

- [High-speed Digital Design: A Handbook of Black Magic](#), Howard Johnson and Martin Graham, Prentice Hall, 1993.
- [Noise Reduction Techniques in Electronic Systems](#), (2nd Ed.), Henry Ott, John Wiley, N.Y., 1998.
- [EMC at the Component and PCB Level](#), Martin O'Hara, Newnes, 1998
- [EMC and the Printed Circuit Board](#), Mark Montrose, IEEE Press, 1998
- [The RF Capacitor Handbook](#), from American Technical Ceramics Inc.
- [The Circuit Designer's Companion](#) , by Tim Williams
- [Reference Data for Engineers](#), 7th edition  
Edward C. Jordan, Editor in chief
- [ABC's of Transformers & Coils](#), by Edward J. Bukstein

# Additional References

- **Reference Application Notes**

- *ADN007, Techniques that Reduce System Noise in ADC Circuits*
- *AN681, Reading and Using Fast Fourier Transforms (FFTs)*
- *AN699, Anti-Aliasing, Analog Filters for Data Acquisition Systems*
- *AN695, Interfacing Pressure Sensors to Microchip's Analog Peripherals*
- *AN688, Layout Tips for 12-Bit A/D Converter Application*
- *AN823, Analog Design in a digital World using Mixed Signal Controllers*

- **At [www.microchip.com](http://www.microchip.com) under ....**

- Analog & Interface Products
  - **FilterLab® Active Filter Design Software**
- EMC Design
  - **EMC 'Webinars'**
  - **EMC Newsletter**

# Trademarks

The Microchip name and logo, the Microchip logo, Accuron, dsPIC, KeeLoq, KeeLoq logo, microID, MPLAB, PIC, PICmicro, PICSTART, PRO MATE, rfPIC and SmartShunt are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

AmpLab, FilterLab, Linear Active Thermistor, Migratable Memory, MXDEV, MXLAB, SEEVAL, SmartSensor and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, Application Maestro, CodeGuard, dsPICDEM, dsPICDEM.net, dsPICworks, ECAN, ECONOMONITOR, FanSense, FlexROM, fuzzyLAB, In-Circuit Serial Programming, ICSP, ICEPIC, Mindi, MiWi, MPASM, MPLAB Certified logo, MPLIB, MPLINK, PICKit, PICDEM, PICDEM.net, PICLAB, PICtail, PowerCal, PowerInfo, PowerMate, PowerTool, REAL ICE, rfLAB, Select Mode, Smart Serial, SmartTel, Total Endurance, UNI/O, WiperLock and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.