

## Solar-array controller needs no multiplier to maximize power


W Stephen Woodward, Chapel Hill, NC

 Solar-photovoltaic arrays are among the most efficient, cost-effective, and scalable “green” alternatives to fossil fuels, and researchers are almost daily announcing new advances in photovoltaic technology. But successful application of photovoltaics still depends on strict attention to power-conversion efficiency. **Figure 1** shows one reason for this attention.

A photovoltaic array’s delivery of useful power to the load is a sensitive function of load-line voltage, which in turn depends on insolation—that is, sunlight intensity—and array temperature. Operation anywhere on the current/voltage curve except at the optimal maximum-power-point voltage results in lowered efficiency and a waste of valuable energy. Consequently, methods for maximum-power-point tracking are common features in ad-

vanced solar-power-management systems because they can boost practical power-usage efficiency—often by 30% or more.

Because of its generality, a popular maximum-power-point-tracking-control algorithm is perturb and observe, which periodically modulates, or perturbs, the load voltage; calculates, or observes, the instantaneous transferred power response; and uses the phase relationship between load modulation and calculated power as feedback to “climb the hill” of the current/voltage curve to the maximum-power-point optimum. The perturb-and-observe algorithm is the basis of the maximum-power-point-tracking-control circuit (**Figure 2**, in yellow) but with a twist (in blue), which achieves a feedback function equivalent to a current-times-voltage power

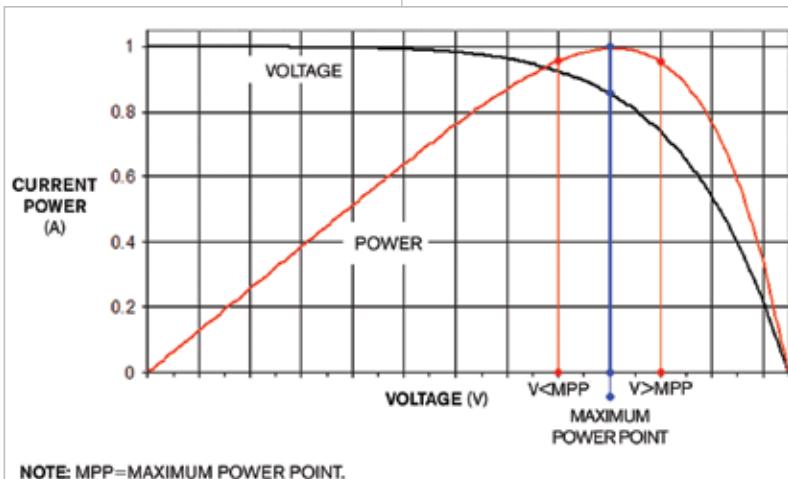

**Figure 1** It is important to operate solar-photovoltaic arrays at their maximum power point.

### DI Inside

**54** Simple microcontroller-temperature measurement uses only a diode and a capacitor

**54** Current mirror drives multiple LEDs from a low supply voltage

 To see all of EDN's Design Ideas, visit [www.edn.com/designideas](http://www.edn.com/designideas).

calculation but without the complexity of a conventional multiplier. The idea relies on the well-known logarithmic behavior of transistor junctions,  $V_{BE} = (kT/q)\log(I_C/I_S) = (kT/q)[\log(I_C) - \log(I_S)]$ , where  $V_{BE}$  is the base-to-emitter voltage. It also relies on the fact that adding logarithms is mathematically equivalent to multiplication. Here’s how.

Capacitor  $C_2$  couples a 100-Hz, approximately 1V-p-p-modulation or 1V-p-p-perturbation square wave from the  $S_2/S_3$  CMOS oscillator onto the photovoltaic-input voltage,  $V$ . The current/voltage curve of the array causes the input current,  $I$ , to reflect the  $V$  modulation with a corresponding voltage-times-current input-power modulation.  $IC_{1A}$  forces  $I_{Q1}$  to equal  $I \times x_1$ , where  $I$  is the solar-array current and  $x_1$  is a gain constant.  $IC_{1B}$  forces  $I_{Q2}$  to equal  $V/499 \text{ k}\Omega$ , where  $V$  is the solar-array voltage. Thus,  $V_{Q1} = (kT_1/q)1[\log(I) - \log(I_{S1}) + \log(x_1)]$ , and  $V_{Q2} = (kT_2/q)[\log(V) - \log(I_{S2}) - \log(499 \text{ k}\Omega)]$ .  $V_{Q1}$  is the base-to-emitter voltage of  $Q_1$ ;  $k$  is the Boltzman constant;  $T_1$  is the temperature of  $Q_1$ ;  $q$  is the elementary charge of the electron;  $I$  is the current input

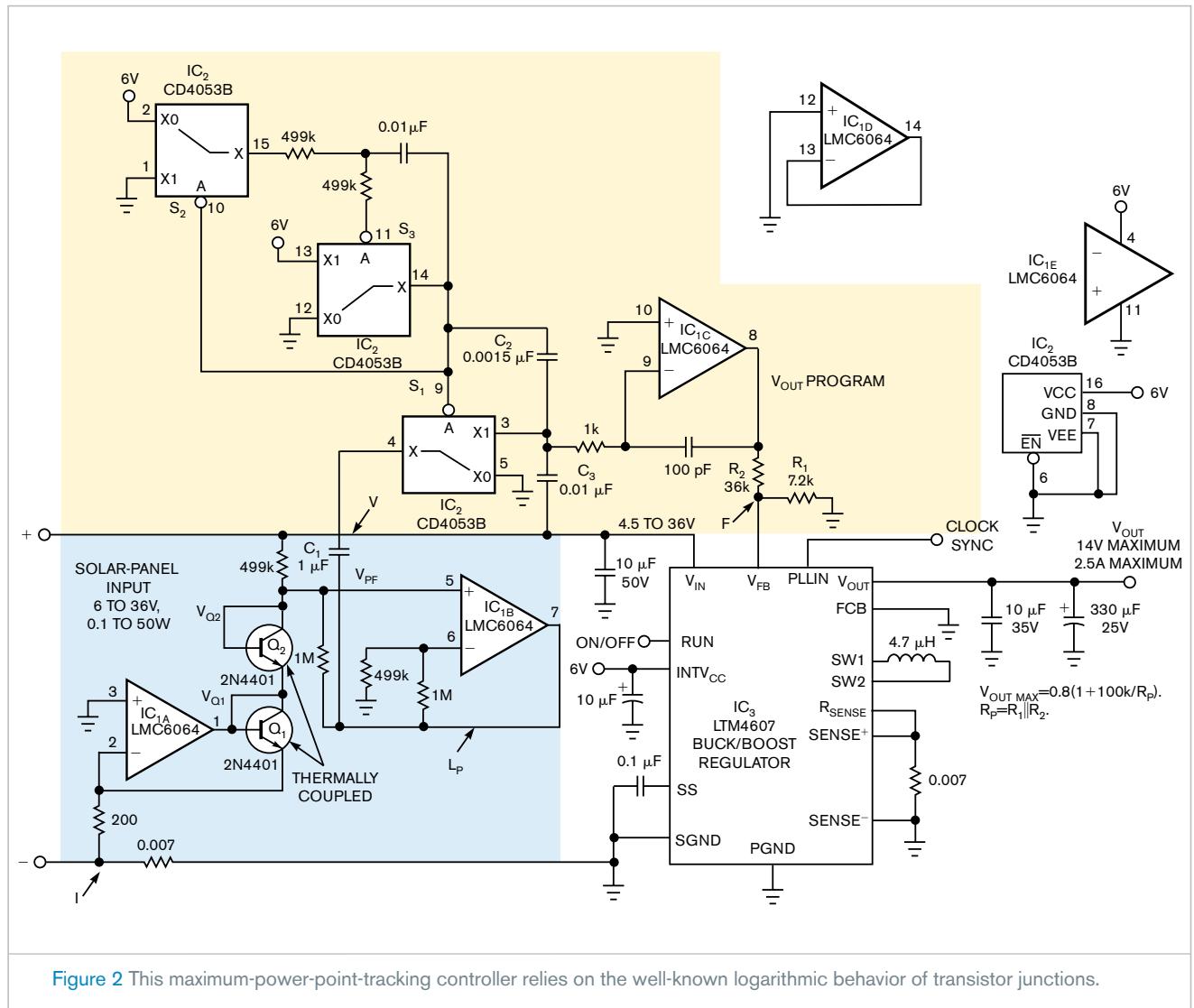


Figure 2 This maximum-power-point-tracking controller relies on the well-known logarithmic behavior of transistor junctions.

from the solar panel's negative terminal;  $I_{S1}$  is the saturation current of  $Q_1$ ;  $x_1$  is the arbitrary gain constant, which  $IC_3$  determines;  $V$  is the voltage input from the solar panel's positive terminal;  $I_{S2}$  is the saturation current of  $Q_2$ ;  $K$  is degrees Kelvin;  $V_{PF}$  is the power-feedback signal; and  $V_{IP}$  is the calculated power-input signal. Because  $k$ ,  $q$ ,  $I_{S1}$ ,  $I_{S2}$ ,  $x_1$ , and  $499\text{ k}\Omega$  are all constants and  $T_1 = T_2 = T$ , however, for the purposes of the perturb-and-observe algorithm, which is interested only in observing the variation of current and voltage with perturbation, effectively,  $V_{Q1} = (kT/q)\log(I)$ , and  $V_{Q2} = (kT/q)\log(V)$ .

The series connection of  $Q_1$  and

$Q_2$  yields  $V_{PF} = V_{Q1} + V_{Q2} = (kT/q) [\log(I) + \log(V)] = (kT/q)\log(VI)$ , and, because of  $IC_{1B}$ 's noninverting gain of three,  $V_{IP} = 3(kT/q)\log(VI) \approx 765\ \mu\text{V}/\%$  of change in watts. The  $V_{IP}$   $\log(\text{power})$  signal couples through  $C_1$  to synchronous demodulator  $S_1$ , and error integrator and control op amp  $IC_{1C}$  integrates the rectified  $S_1$  output on  $C_3$ . The  $IC_{1C}$  integrated error signal closes the feedback loop around the  $IC_3$  regulator and results in the desired maximum-power-point-tracking behavior.

Using micropower parts and design techniques holds the total power consumption of the maximum-power-point-tracking circuit to approximate-

ly 1 mW, which avoids significantly eroding the efficiency advantage—the point of the circuit in the first place. Meanwhile, simplifying the interface between the maximum-power-point-tracking circuit and the regulator to only three connection nodes— $I$ ,  $V$ , and  $F$ —means that you can easily adapt the universal maximum-power-point-tracking circuit to most switching regulators and controllers. Therefore, this Design Idea offers the efficiency advantages of a maximum-power-point-tracking circuit to small solar-powered systems in which more complex, costly, and power-hungry implementations would be difficult to justify. **EDN**

# Simple microcontroller-temperature measurement uses only a diode and a capacitor

Andreas Grün, Wedemark, Germany

Using a PN-junction diode for temperature measurement usually depends on its 2-mV/K temperature coefficient. Conventionally, you must amplify and digitize this voltage with an ADC before you can use the value in a microcontroller. Less well-known is the fact that the reverse current of a PN-junction diode shows a good exponential dependency over temperature; increasing the temperature by approximately 12K doubles the

leakage (Figure 1). An easy way to measure current over such a large range of two to three decades is to charge and discharge a capacitor and measure the time or frequency.

A general-purpose I/O pin of a microcontroller charges a capacitor either by using it temporally as an output or by enabling a pull-up resistor, which is available in some controllers (Figure 2a). After charging the pin, you configure it as a high-impedance

input, and a capacitor discharges through the leakage current of the diode (Figure 2b). The discharge time then is proportional to the temperature of the diode; thus, the diode exhibits exponential behavior. Depending on the type of diode, the exponential behavior can be nearly ideal. Calibration of a base point is necessary because the absolute value of the current varies greatly at a given temperature.

Selecting the diode and the value of the capacitor requires some care. The smaller the PN junction,

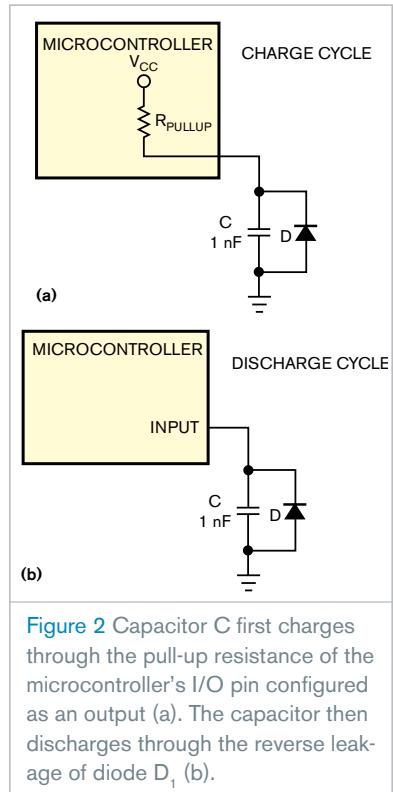


Figure 2 Capacitor C first charges through the pull-up resistance of the microcontroller's I/O pin configured as an output (a). The capacitor then discharges through the reverse leakage of diode D<sub>1</sub> (b).

the smaller the reverse current and the longer the discharging time. Periods longer than a few seconds are usually unsuitable. Making the capacitor's value too low leads to errors because the capacitance of any cable and the capacitance of the PN-junction diode come into effect.

Typically, a power diode, such as a 1N4001 with a capacitance of 1 nF, gives suitable results. The discharge time is approximately 0.3 to 1 sec at room temperature, falling into the millisecond range at 100°C. The PN-junction diode of a power transistor should also work. **EDN**

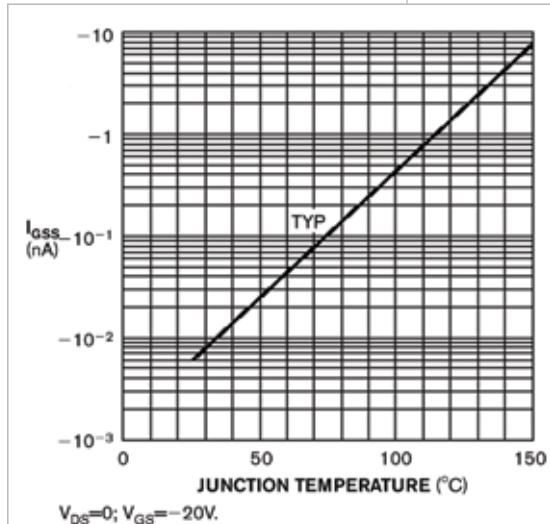


Figure 1 The reverse current of a PN-junction diode shows an exponential dependency over temperature; increasing the temperature by approximately 12K doubles the leakage.

# Current mirror drives multiple LEDs from a low supply voltage

Rex Niven, Forty Trout Electronics, Eltham, Victoria, Australia

Driving LEDs at a regulated current from low supply voltages can be difficult because minimal

overhead voltage is available for control circuits. A current-mirror architecture is suitable but usually works only

with ICs with well-matched transistors and in which the silicon substrate holds them at one temperature. However, high currents—approximately 100 mA—are not normally possible. A thermal runaway can occur in circuits using unfavorable combinations of discrete bipolar transistors. In this scenario, one LED-driver transistor becomes

slightly hotter than the others, its gain increases, and it takes more current and gets even hotter until it self-destructs. This Design Idea shows how you can avoid this problem for pulsed-current-mirror applications.

The current mirror comprises  $Q_4$  through  $Q_7$  with connected bases and emitters, and the collector current of  $Q_3$  is the control output (Figure 1). Resistor  $R_3$  converts  $Q_3$ 's collector current to a feedback voltage. Transistors  $Q_1$  and  $Q_2$  form a voltage-difference amplifier. The control-transistor current after feedback is  $1.2V/R_3$ , and the LEDs have a similar current. Because of the pulsed operation—say, 25% duty at 3 Hz—the transistor temperature does not reach a stable value

and cools again toward the ambient temperature during the off period. The thermal-runaway effect does not have time to develop.

The capacitor prevents transient oscillations at switch-on or -off. Use the same transistor type for  $Q_4$  through  $Q_7$

and mount all of them on the same part of the PCB (printed-circuit board). The supply voltage can be as low as 2.5V for certain LEDs, especially infrared types, and the collector current can exceed 100 mA per LED. **EDN**

