

end of each period, a positive-going edge appears at F. Each positive edge at F makes counter IC₂ count down by one.

When the circuit has produced N periods at S, the voltage at C goes high, which indicates end of count. The voltage at D goes high and disables the counter. IC_{3C} and IC_{3D} invert the voltage at D, and the resulting 0V drive turns on

Q₁. A 5V level is present at E, and IC₄ switches are on. The internal oscillator of IC₁ stops, and the output signal at F returns to zero. Before returning to the original state, the signal at B should return to zero, which happens after the end of the delay that one-shot IC_{5A} produces.

All is now ready for another train of pulses. Using S₁, you can program the cir-

cuit for one to 15 pulses. The circuit can produce other signal shapes, depending on how you connect A₀ and A₁ of IC₁ (Table 1). You can also replace S₁ with a μC to produce any pattern of pulses.

Is this the best Design Idea in this issue? Vote at www.ednmag.com/ednmag/vote.asp.

High-voltage current-feedback amplifier is speedy


Joseph Ting, Institute of Atomic and Molecular Sciences of the Academia Sinica, Taipei, Taiwan

THE CIRCUIT IN FIGURE 1 powers a microparticle and nanoparticle ion trap through a 1-to-5-turns-ratio, high-voltage transformer. It also works successfully as a driver for a piezo-tube scanner and in a near-field scanning optical microscope. The circuit is robust and works with supplies ranging from ±50 to ±230V. The measured parameters at ±230V supply voltage are gain of 26-dB from dc to -3-dB point at 7 MHz; output swing of ±200V, rise and fall times of 70 nsec for an output step of 350V, slew rate of 4100V/μsec, and supply current of 56 mA.

The red LEDs, D₁ and D₂, in Figure 1 provide a 1.8V drop; the LEDs are more rugged than precision IC voltage references. The current supply for IC₁ comes from R₁ and the source comprising D₁, R₂, R₃, and Q₁. R₃'s trimmed value is such that Q₂'s quiescent current is approximately 15 mA. You can determine this current by measuring the voltage drop across R₄. The same adjustment also controls the output-voltage offset. IC₂ is a unity-gain, high-current driver for Q₂. D₃ prevents IC₂'s input from going more negative than its negative supply. Q₃, D₄, C₁, and R₅ provide the negative bias for IC₂. Q₄ is an output-current limiting switch. Q₄ starts to turn on at I_{OUT}=290 mA. You can replace the bipolar transistors C3955 (npn, Q₂ and Q₆) and A138 (pnp, Q₃ and Q₇) by equivalents as long as they have the following minimum specs: V_{CEO}≥250V; I_C≥100 mA, and f_T≥100 MHz.

You should mount all the power tran-

Figure 1

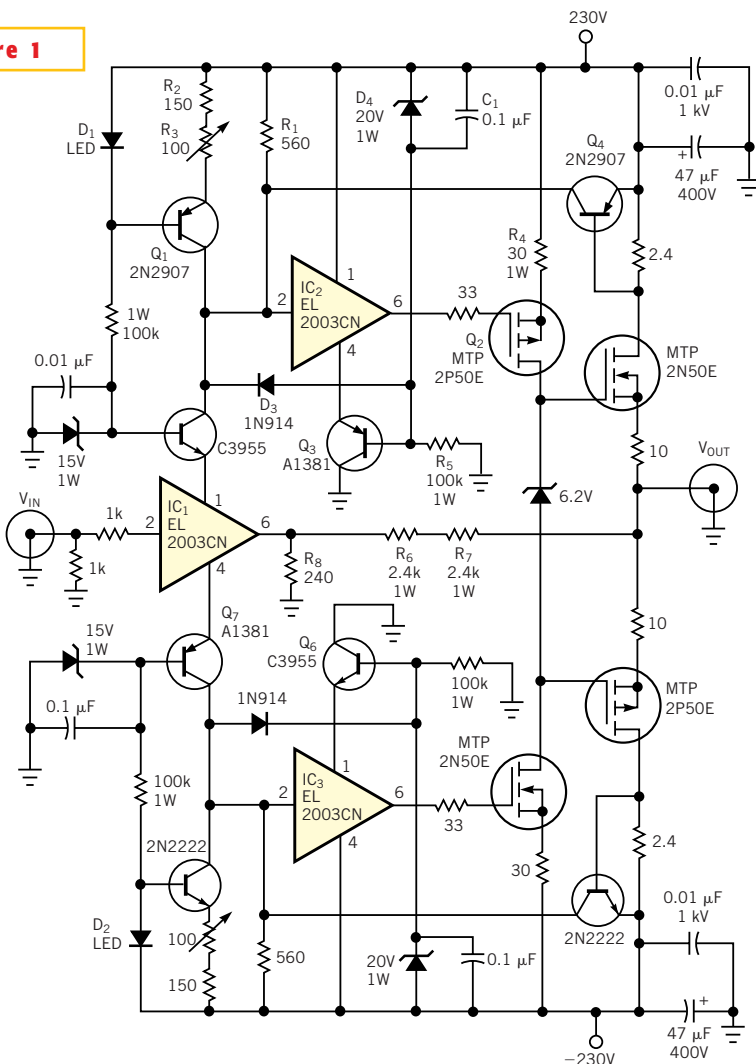

This high-voltage, current-feedback amplifier slews at 4100V/μsec.

sistors in individual finned heat sinks with an overhead 3-in. fan for cooling. The pc-board layout is not critical and needs no ground plane. However, you must use single-point grounding to minimize ringing. For the component values shown, the circuit is very stable and needs no compensation capacitors. **Figure 2** shows a large-signal response for a $\pm 9V$, 1-MHz square-wave input. This circuit has a fixed gain of 20. For higher gains, you can increase the values of R_6 and R_7 . For lower values, it is better to insert an attenuator at the input, because smaller values of R_6 and

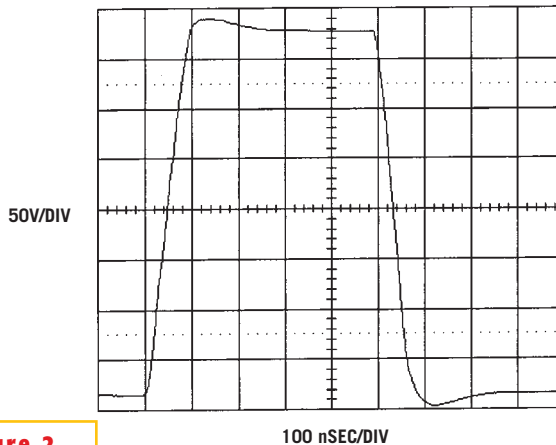


Figure 2

The circuit has a clean square-wave response with minimal overshoot and no ringing.

R_7 may result in excessive dissipation. Do not change the value of R_8 , because it is optimized for speed. Be cautious when measuring and using this circuit, because it harbors lethal voltages. The National Science Council of Taiwan sponsored this project.

Is this the best Design Idea in this issue? Vote at www.edn.com/ednmag/vote.asp.

AC-power monitor uses remote sensing

Sanjay R Chendvankar, Tata Institute of Fundamental Research, Colaba, Mumbai, India

THE DETECTION CIRCUIT in the Design Idea “Circuit monitors ac-power loss” (*EDN*, Nov 24, 1999, pg 172) requires a physical connection with the mains to sense the power loss. The circuit in **Figure 1** senses the power loss through the radiated power-line signal. The battery-operated circuit has a quiescent-current drain of approximately $2 \mu A$. The antenna, which is either a telescopic antenna or simply an approximately 2-ft-long wire, intercepts the radiated power-line signal. The CMOS inverters, IC_{1A} and IC_{1B} , amplify this weak signal and convert it into a digital signal. D_1 and C_1 generate a steady dc voltage at the input of IC_{1C} . D_1 prevents discharge of C_1 through the output of IC_{1B} when the square wave at this output periodically goes to a low level. Inverters IC_{1D} , IC_{1E} , and IC_{1F} connected in parallel enhance the current-sink capacity for sinking the piezo-buzzer current. When the ac mains is present, the output of IC_{1C} is

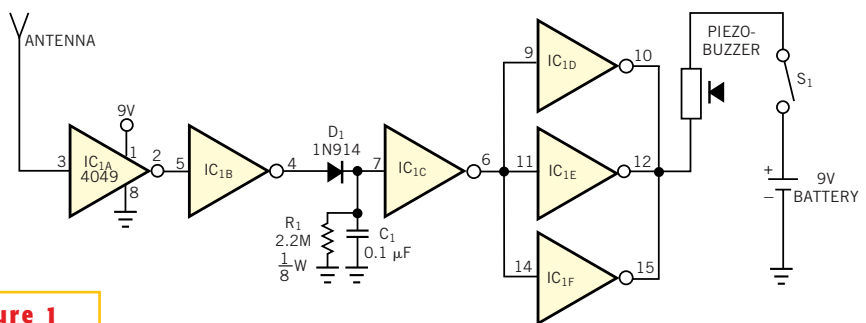


Figure 1

A low level at the outputs of IC_{1D} , IC_{1E} , and IC_{1F} activates the piezo-buzzer and warns of ac-line failure.

low; hence, the levels of IC_{1D} , IC_{1E} , and IC_{1F} are high, and the buzzer is off. When the ac power fails, the output of IC_{1B} goes low; C_1 discharges through R_1 ; and IC_{1D} , IC_{1E} , and IC_{1F} go low. This level activates the piezo-buzzer and warns of ac-line failure. Switching off the battery power

deactivates the buzzer. You can turn S_1 on after ac power resumes.

Is this the best Design Idea in this issue? Vote at www.edn.com/ednmag/vote.asp.