

Bipolar Stepper Motor

This design implements a controller for a bipolar stepper motor using the L297 controller and L298 driver ICs

Note that the L297 can drive the motor both clockwise and anti-clockwise, and also provides a reset function which returns the rotor to the home position.

