

# Gate Drive Optocoupler Basic Design for IGBT / MOSFET Applicable to All Gate Drive Optocouplers



## Application Note 5336

### 1. Introduction

This application note covers the topic of calculating gate driver power and thermal dissipation of the gate drive optocoupler IC. Gate drive optocouplers are used to drive, turning-on and off, power semiconductor switches, MOSFETs / IGBTs. The gate drive power calculation can be divided into three parts; power consumed or lost in the internal circuitry of the driver, power sent to the power semiconductor switches (IGBT/MOSFET) and power lost at the external component between the driver IC and the power semiconductor switch, e.g. across external gate resistor. In the following example, we will discuss a IGBT gate driver design using Avago ACPL-332J (2.5A peak intelligent gate driver). This design guide is applicable for MOSFET gate driver.

### 2. IGBT/MOSFET Gate Resistor

When choosing the value of  $R_G$ , it is important to look from the point from both gate driver IC and the power semiconductor switches, MOSFET / IGBT. For the gate driver IC, we choose an  $R_G$  that is within the IC maximum allowable power dissipation rating while sourcing/sinking the highest possible driver current. From the IGBT or MOSFET point of view, the gate resistor influences the voltage change  $dV_{CE}/dt$  and current change  $di_C/dt$  during the turn on and turn off period.

So it is important when a designer chooses an IGBT or MOSFET, the appropriate gate driver optocoupler is also chosen as the current and power rating of this driver determine how fast the IGBT or MOSFET is turn-on and turn-off.

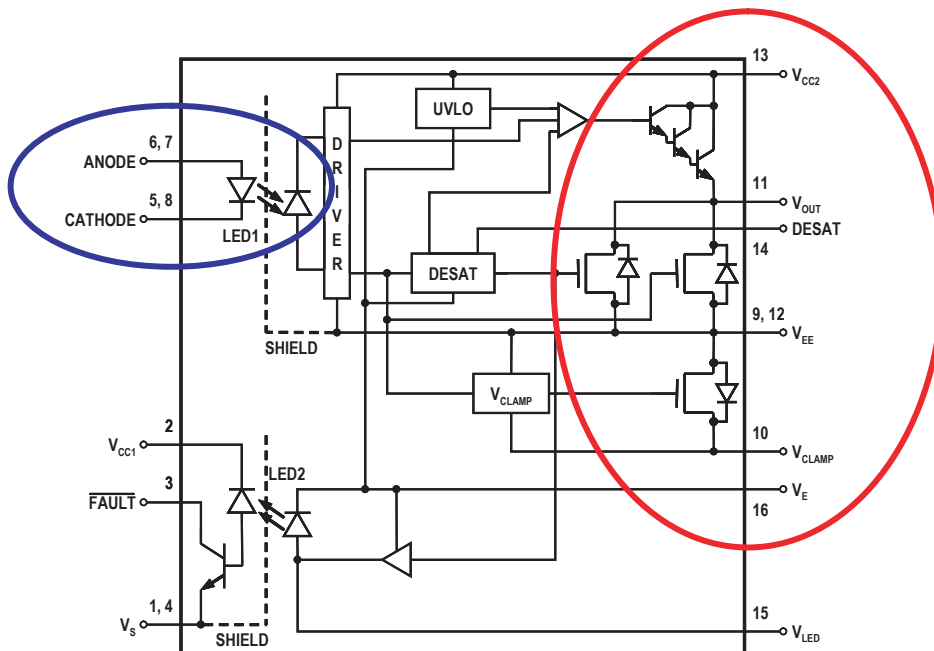


Figure 1. Block Diagram of ACPL-332J

### 3. Gate Drive Power Operation within IC Maximum Allowable Power Ratings

The power dissipation of the gate drive optocoupler is a combination of output-side power to IGBT/MOSFET, red circle and the input-side power due to input LED power dissipation, blue circle. The power dissipation for second LED used in fault feedback is neglected as the current to drive the open-collector transistor is small.

The calculation steps are:

1. Calculate the minimum desired  $R_G$  according to the maximum peak gate current
2. Calculate total power dissipation
3. Compare the input and output power dissipation calculated in step #2 to the maximum recommended dissipation for the IC. (If the maximum recommended level has been exceeded, it may be necessary to raise the value of  $R_G$  to lower the switching power and repeat step #2.)

In this example, the total input and output power dissipation of ACPL-332J is calculated given the following conditions:

- $I_G = I_{ON, MAX} \sim 2.5 \text{ A}$
- $V_{CC2} = 18 \text{ V}$
- $V_{EE} = -5 \text{ V}$ , (Note:  $V_{EE} = 0\text{V}$  if negative voltage supply is not required in application)
- $f_{SWITCH} = 15 \text{ kHz}$
- Ambient Temperature =  $70^\circ\text{C}$

#### Step I: Calculate $R_G$ minimum from $I_{OL}$ peak specification:

To find the peak charging  $I_{OL}$  assume that the gate is initially charged the steady-state value  $V_{EE}$ . For ACPL-332J, the voltage drop is linearly approximated as 4.5V for 2.5A output at  $70^\circ\text{C}$  (Fig 2:  $V_{OL}$  vs  $I_{OL}$ ). Therefore apply the following relationship:

 


Figure 2.  $V_{OL}$  vs  $I_{OL}$

$$I_{OL, PEAK} = 2.0\text{A @ } 4.5\text{V internal voltage drop}$$

$$R_g = \frac{V_{CC2} - V_{EE} - V_{OL}}{I_{OL}} = \frac{18\text{V} - (-5\text{V}) - 6.3}{2.5 \text{ A}} = 6.68 \Omega \text{ (approximately } 6.8 \Omega)$$

Note: The value of the gate resistance has a significant impact on the dynamic performance of IGBTs/MOSFETs. A smaller gate resistor charges and discharges the power transistor input capacitance faster reducing switching times and switching losses. The trade off is that this could lead to higher voltage oscillations. In the MOSFET and IGBT datasheet, there is usually a recommended gate resistor which is used for the datasheet characterization. However, designer should be cautious not to over-drive the gate drive IC using the recommended gate resistance from the IGBT or MOSFET datasheet.

#### Step II: Calculate total power dissipation in the gate driver:

The total power dissipation ( $P_T$ ) is equal to the sum of the input-side power ( $P_I$ ) and output-side power ( $P_O$ ) dissipation:

$$P_T = P_I + P_O$$

$$P_I = I_{F(ON), max} * V_{F, max}$$

where,

$$I_{F(ON), max} = 12\text{mA}$$

$$V_{F, max} = 1.95\text{V}$$

The  $I_{F(ON)}$  can be found in the recommended operating conditions and  $V_F$  can be found in ACPL-332J datasheet, Table 5 of the electrical specifications.

#### Electrical Specification

	Min	Typ	Max	Units
Input Forward Voltage, $V_F$	1.2	1.6	1.95	V

$$P_O = P_{O(BIAS)} + P_{O(SWITCH)}$$

$$= I_{CC2, MAX} * (V_{CC2} - V_{EE}) + \Delta V_{GE} * Q_G * f_{SWITCH}$$

where,

$P_{O(BIAS)}$  = steady-state power in the driver due to biasing the device.

$P_{O(SWITCH)}$  = Driver power for charging and discharging of device gate capacitances.

$I_{CC2, MAX}$  = Supply Current to power internal circuitry

$$\Delta V_{GE} = V_{CC2} + |V_{EE}|$$

$Q_G$  = Total gate charge of the IGBT or MOSFET as described in the manufacturer specification (Illustrated in Figure 3) = 240nC (approximation for a 100A IGBT)

$f_{SWITCH}$  = switching frequency of application

Using the above information, we calculate both  $P_I$  and  $P_O$  below

$$P_I = 12 \text{ mA} * 1.95 \text{ V} = 23.4 \text{ mW}$$

$$\begin{aligned} P_O &= P_{O(\text{BIAS})} + P_{O(\text{SWITCH})} \\ &= 5.0 \text{ mA} * (18 \text{ V} - (-5 \text{ V})) + (18 \text{ V} + 5 \text{ V}) * 240 \text{ nC} * 15 \text{ kHz} \\ &= 115 \text{ mW} + 82.8 \text{ mW} \\ &= 197.8 \text{ mW} \end{aligned}$$

 


Figure 3. Typical IGBT Gate Charge Curve

### Step III: Compare the calculated power dissipation with the absolute maximum values in the IC:

For the ACPL-332J, the maximum power dissipation can be found in Table 3 of the ACPL-332J data sheet. Absolute Maximum rating in AV02-0120EN data sheet. Also, it requires derating of 10mW/°C if the operating temperature is above 90°C (Note. 2 ACPL-332J datasheet).

#### Absolute Maximum Rating

	Min	Max	Units
Output IC Power Dissipation, $P_O$		600	mW
Input IC Power Dissipation, $P_I$		150	

$$P_I = 23.4 \text{ mW} < 150 \text{ mW (abs. max.)} \quad \text{OK}$$

$$P_O = 197.8 \text{ mW} < 600 \text{ mW (abs. max.)} \quad \text{OK}$$

Therefore, the power dissipation absolute maximum rating has not been exceeded for the above example.

Note: Heat dissipation for different packages require derating when the operating temperature exceed a certain level. For ACPL-332J, as operating temperature is below 90°C, derating is not necessary. Operating temperature is different for different products

Another method to check if the device is within the maximum limits is to calculate the junction temperature of the device. We continue to use the example provided earlier.

$$\text{Power dissipation, } P_D = 23.4 + 197.8 = 221.2 \text{ mW}$$

The output detector junction temperature is given by

$$T_J = P_D * (\theta_{J-P} + \theta_{P-A}) + T_A$$

Using the  $\theta_{J-P} = \theta_{9-12} = 30^\circ\text{C/W}$  (ACPL-332J Table 7. Package Characteristic) and  $T_A$  of  $70^\circ\text{C}$  and assuming the thermal resistance from pin to ambient,  $\theta_{P-A}$  is  $50^\circ\text{C/W}$

$$T_J = 197.8 * (30 + 50) + 70^\circ\text{C} = 85.8^\circ\text{C}$$

If the junction temperature is higher than the maximum junction temperature rating (in this case  $125^\circ\text{C}$ ), the desired specification must be derated according.

Designers should note that the thermal resistance between pin to ambient is also the PCB heatsink thermal resistance. This thermal resistance is then dependent on the area size on the PCB and the free air-flow.

### Further Topics:

#### Higher Output Current Using an External Current Buffer:

To increase the IGBT gate drive current, a non-inverting current buffer (such as the npn/pnp buffer shown in Figure 75 of HCPL-316J data sheet) may be used. Inverting types are not compatible with the desaturation fault protection circuitry and should be avoided. To preserve the slow IGBT turn-off feature during a fault condition, a 10 nF capacitor should be connected from the buffer input to  $V_{EE}$  and a 10Ω resistor inserted between the output and the common npn/ pnp base. The MJD44H11/ MJD45H11 pair is appropriate for currents up to 8A maximum. The D44VH10/ D45VH10 pair is appropriate for currents up to 15 A maximum.

#### Thermal Model

Most of the steady state thermal model of gate drive optocouplers can be found in AN1087. The thermal resistance values given in this model can be used to calculate the temperatures at each node for a given operating condition.

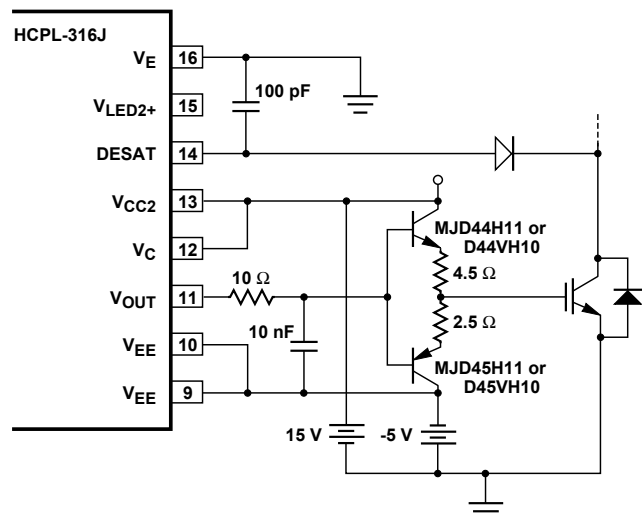


Figure 4. Current buffer for increased drive current.

### Printed Circuit Board Layout Considerations

Adequate spacing should always be maintained between the high voltage isolated circuitry and any input referenced circuitry. Care must be taken to provide the same minimum spacing between two adjacent high-side isolated regions of the printed circuit board. Insufficient spacing will reduce the effective isolation and increase parasitic coupling that will degrade CMR performance.

The placement and routing of supply bypass capacitors requires special attention. During switching transients, the majority of the gate charge is supplied by the bypass capacitors. Maintaining short bypass capacitor trace lengths will ensure low supply ripple and clean switching waveforms.

Figure 5 below shows example PCB layout using HCPL-316J gate driver optocoupler. Ground Plane connections

are necessary for pin 4 (GND1) and pins 9 and 10 ( $V_{EE}$ ) in order to achieve maximum power dissipation as the HCPL-316J is designed to dissipate the majority of heat generated through these pins. This is also applicable for ACPL-332J. For this case, the ground plane connections are pin 1, pin 4 ( $V_{SS}$ ) and pin 4 ( $V_{SS}$ ), pin 9 and 12 ( $V_{EE}$ ). Actual power dissipation will depend on the application environment (PCB layout, air flow, part placement, etc.) See Application Note 1087 section for details on how to estimate junction temperature.

The layout examples in Figure 5 have good supply bypassing and thermal properties, exhibit small PCB footprints, and have easily connected signal and supply lines. The four examples cover single sided and double sided component placement, as well as minimal and improved performance circuits.

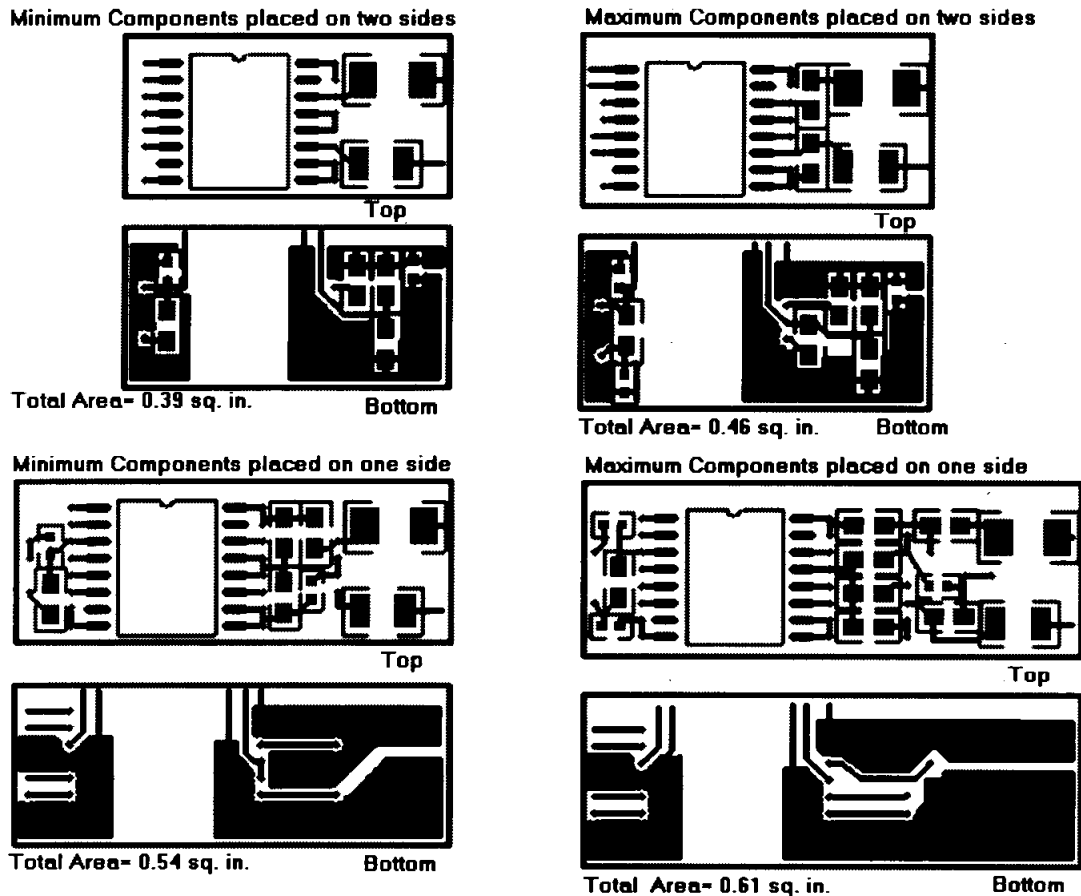


Figure 5. Recommended layout(s)

For product information and a complete list of distributors, please go to our web site: [www.avagotech.com](http://www.avagotech.com)